


L10 Circuits, E.M.F., Power & Model of resistance

Last time we learned that the fluid of electricity is made up of electrons or holes, moving at an incredibly high velocity. The scattering of these electrons inside the metal means that their average drift velocity is only a fraction of a mm per second.

Today we will discuss how we set up a constant current inside a metal, and this will involve the concept of a circuit - literally a closed "loop" around which electrical current can flow. We'll also learn about "Electro-motive force" - actually the driving voltage that pumps charge around a circuit.

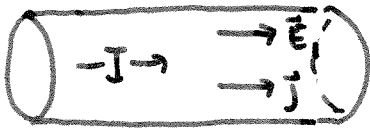25.4

In order for electrons to flow, they need a complete circuit. If a circuit is broken, charge quickly builds up at the end of the wire, producing an electric field which cancels the external electric field



a)




b)

Build up of charge at ends of broken circuit produces a field \vec{E}_2 which exactly cancels the external field.

25.4 E.M.F.


When a current flows through a resistor, it flows from "high" to "low" voltage. The voltage drop is given by

$$V_{ab} = IR$$

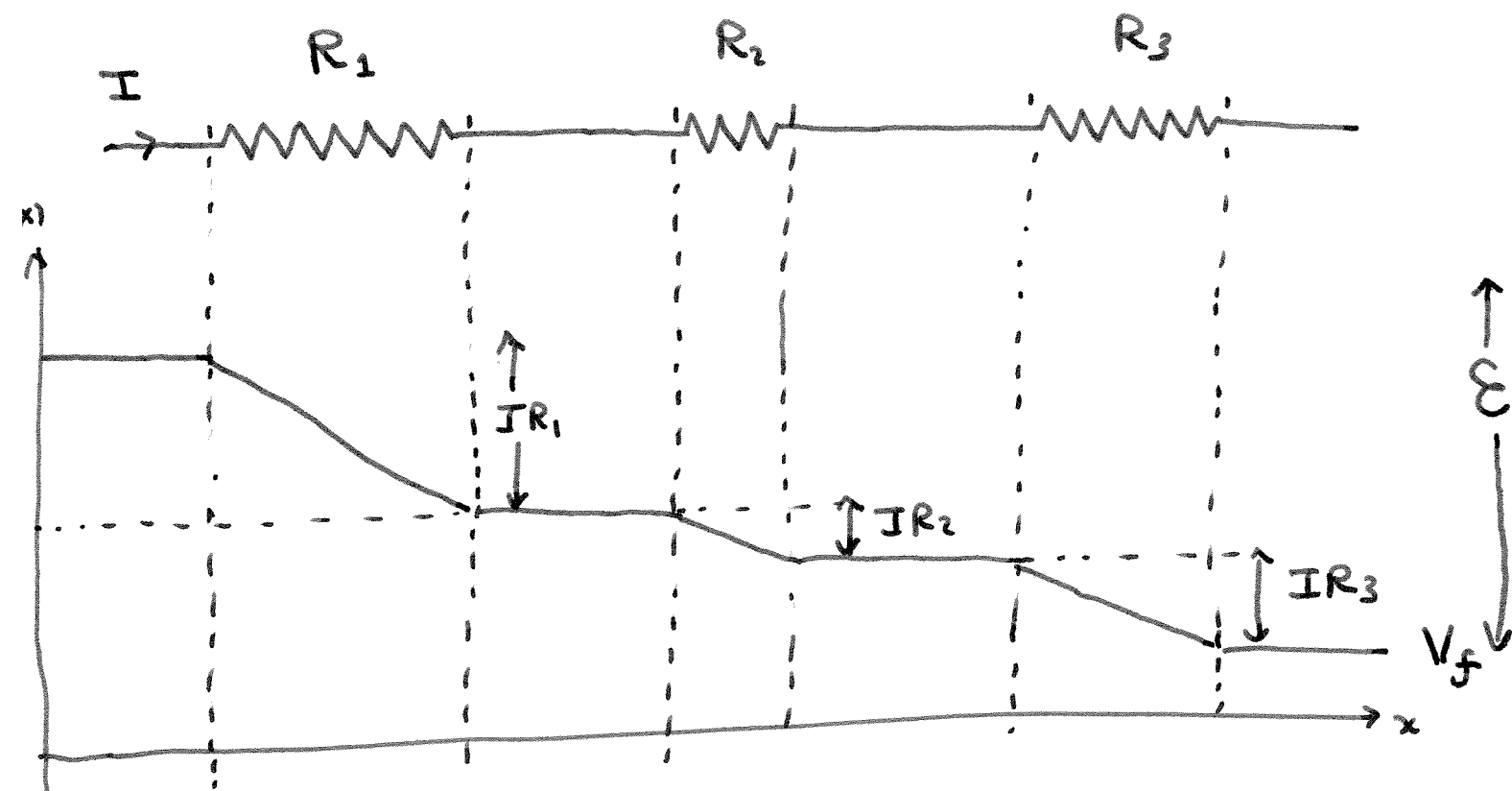

Its a little like running "downhill".

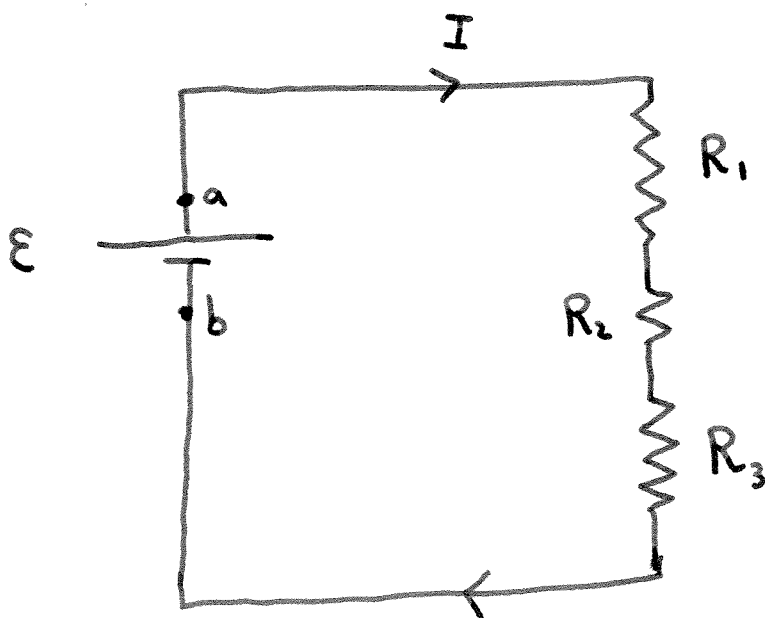At some point one needs a "pump" in the circuit to bring the charged particles back up to the starting potential. The difference between the starting & finishing potential is the electro-motive force, or E.M.F. In a circuit diagram we would draw this as follows



$$V_{ab} = \mathcal{E}$$

and we write

$$\mathcal{E} = IR_1 + IR_2 + IR_3 = IR$$



$$R = R_1 + R_2 + R_3$$

Internal resistance

In practice, all E.M.F sources (batteries, solar cells, thermocouples, fuel cells) have an internal resistance. We label this as " r ". When a current flows, the internal resistance r reduces the output voltage

$$V_{ab} = \mathcal{E} - Ir$$

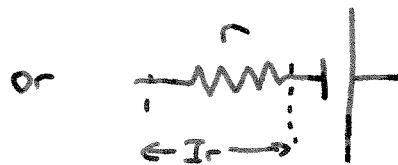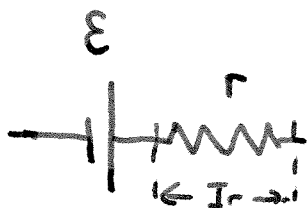We denote such a battery by the circuit diagram



$$\mathcal{E} = \underset{\substack{\uparrow \\ \text{internal} \\ \text{resistance}}}{Ir} + \underset{\substack{\uparrow \\ \text{external} \\ \text{resistance}}}{IR}$$

$$I = \frac{\mathcal{E}}{R + r}$$

SYMBOLS FOR CIRCUIT DIAGRAMS



conductor with negligible resistance

R



Resistor



E.M.F. source



E.M.F. source + internal resistance



Voltmeter (measures potential difference)




Ammeter (measures current through it)



Capacitor C



Inductor L

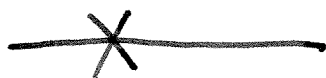

Josephson Junction.


e.g. Source on open circuit. Battery with EMF $\mathcal{E} = 10\text{V}$ & internal resistance $r = 3\Omega$. What is

a) current + voltage in an open circuit?

b) current + voltage when connected in series with a 7Ω resistor?

c) current & voltage when short-circuited?

a)

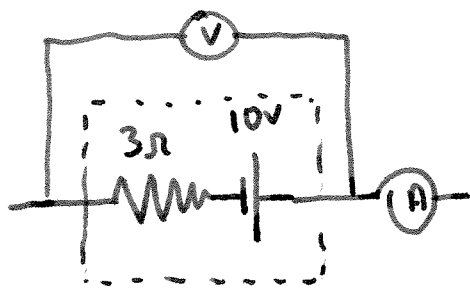


Open circuit

$I = 0$ on Ammeter

$$V_{ab} = \mathcal{E} - I r = \mathcal{E} = 10\text{V}$$

b)

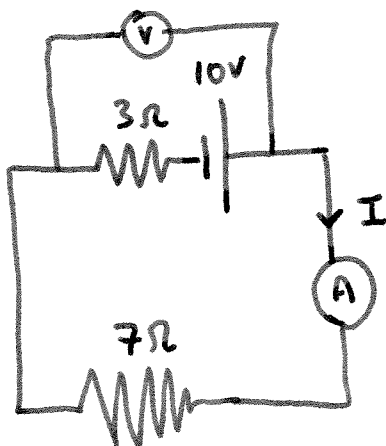

$$\mathcal{E} = I (r + R)$$

$$= I (10\Omega)$$


$$\Rightarrow I = \frac{\mathcal{E}}{10} = \underline{1\text{A}}$$

$$V_{ab} = \mathcal{E} - I r$$

$$= 10 - 1 \times 3\Omega$$

$$= \underline{7\text{V}}$$

c)

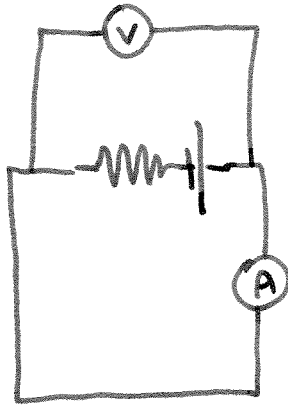


Short circuit

$$I = \frac{\mathcal{E}}{r+R} = \frac{\mathcal{E}}{r} = \frac{10\text{V}}{3\Omega} = 3.3\text{A}$$

$$V = \mathcal{E} - Ir = 0.$$

25.5 ENERGY + POWER

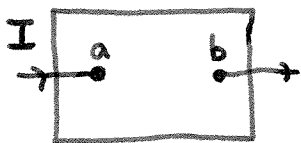

$$\text{Work done on device} = dq V_{ab} = dq(V_a - V_b) = dW$$

$$dq = I dt$$

$$dW = dq V_{ab} = I V_{ab} dt$$

$$P = \frac{dW}{dt} = I V_{ab}$$

$$(1 \text{ C/s})(1 \text{ J/C}) = 1 \text{ J/s} = 1 \text{ W}$$

WATT

For a pure resistor,

$$P = I V_{ab} = I^2 R = \frac{V_{ab}^2}{R}$$

Source - power output.



$$P = I V_{ab}$$
$$= I (\mathcal{E} - I r)$$


$$= \mathcal{E} I - I^2 r$$

↑
loss to internal
resistance

Source - power input (e.g. charging laptop battery).

$$V_{ab} = \mathcal{E} + I r$$

$$P = V_{ab} I = \mathcal{E} I + I^2 r$$

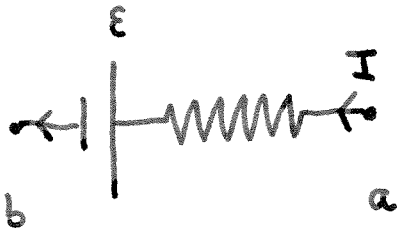

$$\mathcal{E} I = P - I^2 r$$

↑
input power

↑
loss to internal resistance.


↑
rate of conversion from electrical to chemical energy.

e.g Power output from a source. Find

(a) rate of energy conversion (chemical to electrical)

(b) rate of dissipation of energy in battery.

(c) power output.

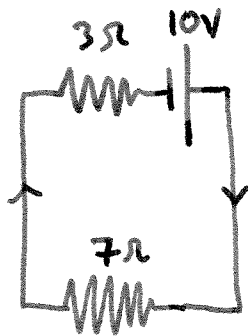

$$I = \frac{\mathcal{E}}{r+R} = \frac{10}{10} = 1\text{A}$$


a) $\mathcal{E}I = 10 \times 1 = 10\text{W}$

b) $I^2 r = (1 \times 1) \times 3 = 3\text{W}$

c) $P = I^2 R = 7\text{W}$.

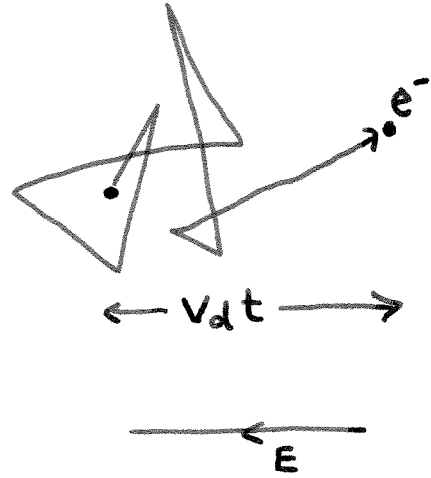25.6 Drude Model for Resistivity.

In an electric field, electrons acquire a drift velocity \vec{v}_d . The current density is then



$$\vec{J} = nq\vec{v}_d$$

Now we know that the electron accelerates in a field with an acceleration

$$\vec{a} = \frac{\vec{F}}{m_e} = \frac{q\vec{E}}{m_e}$$

The velocity after a time t is

$$\vec{v} = \vec{v}_0 + \vec{a}t$$

The average of this quantity, $v_d = \langle v \rangle = \langle v_0 \rangle + a \langle t \rangle$, is the drift velocity.

But the average velocity after a collision is zero $\langle v_0 \rangle = 0$ and the average time between collisions $\langle t \rangle = \tau$, the collision time, so

$$\vec{v}_d = \vec{a}\tau = \frac{q\vec{E}}{m}\tau$$

and hence the current density is

$$\vec{J} = \frac{nq^2\tau}{m}\vec{E}$$

But $\vec{J} = \frac{1}{\rho}\vec{E}$ where ρ is the resistivity, so

$$\rho = \frac{m}{ne^2\tau}$$

DRUDE FORMULA.

e.g Calculate the scattering time τ for

silver, where $\rho = 1.47 \times 10^{-8} \Omega m$ and

$$n_e = 5.9 \times 10^{28} m^{-3}.$$

$$\rho = \frac{m}{ne^2\tau} \Rightarrow \tau = \frac{m}{ne^2\rho}$$

$$\tau = \frac{9.1 \times 10^{-31} \text{ kg}}{(5.9 \times 10^{28} m^{-3})(1.6 \times 10^{-19})^2 (1.47 \times 10^{-8} \Omega m)}$$

$$= 4.1 \times 10^{-14} s$$

About 2.5×10^{13} or

25,000,000,000,000

collisions per second!