

L12

Today we'll talk of two things. We'll begin by discussing how we measure current, voltage & resistance. If you go to Radio Shack or Home Depot, you can pick up a small device called a "multimeter" which measures all these things. What's inside it?

We'll then turn to take our first look at a "dynamical circuit": a circuit in which the current changes with time. Today we will look at an "RC circuit", a circuit in which a capacitor

& a resistor are connected in series. We'll see that the way a capacitor discharges is very reminiscent of radio-active decay. Each RC circuit has a "half life" — or alternatively a "time constant" — which determines the time required for the charge to decay (by a given factor).


16.3

ELECTRICAL INSTRUMENTS


- i) • Ammeter
 - ii) • Voltmeter
 - iii) • Ohmmeter
- } "Multimeter"

iv) • Potentiometer

i) Basic detection system
"Galvanometer"

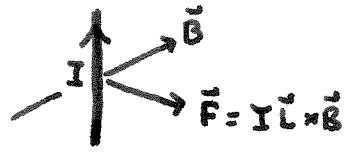

Magnetic Force on Current.

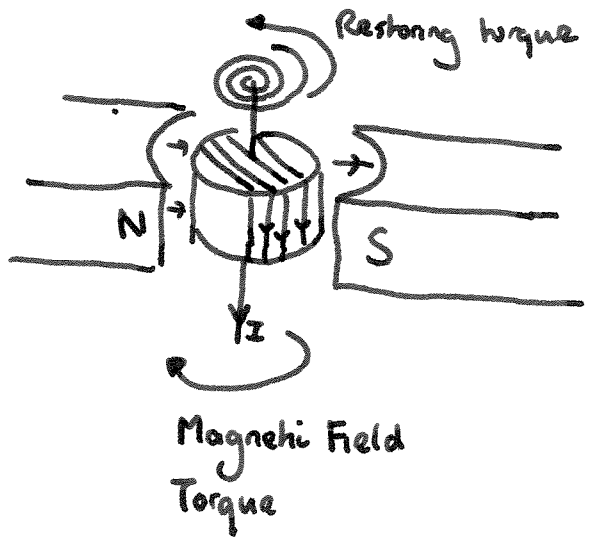

Deflection \propto current

Voltage drop

$$V = I_{fs} R_c$$

↑
coil


e.g. $1\text{mA } 20\Omega \Rightarrow 20\text{mV}$

Always some voltage drop across a Galvanometer.

Galvanometer can be used for both current + voltage measurement

- Changing current range of Galvanometer

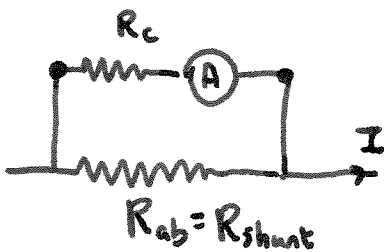e.g. suppose $R_c = 20\Omega$, $I_{fs} = 1\text{mA}$ & want to measure a maximum of 10mA .



$$V = I_{fs} R_c$$

$$= (I - I_{fs}) R_{ab}$$


$$\Rightarrow I_{fs} (R_c + R_{ab}) = I R_{sh}$$

$$\frac{R_{ab} + 1}{R_{sh}} = \frac{I}{I_{fs}}$$

$$\frac{I}{I_{fs}} = 10 \quad \frac{R_{ab}}{R_{sh}} = 9$$

$$R_{ab} = 20\Omega \quad R_{sh} = \frac{20}{9} \Omega = 2.2\Omega$$

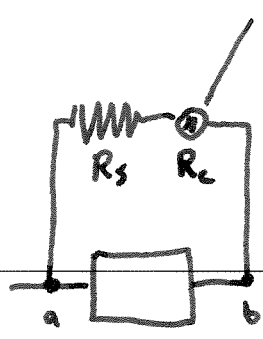ii) Galvanometer in voltage measuring mode



full swing voltage
 \downarrow
 $V_{ab} = (R_s + R_c) I_{fs}$

full swing current.
 \downarrow
 I_{fs}

e.g: How do we make a voltmeter with a max range 50.0V out of a Galvanometer with $R_c = 20\Omega$ & $I_{fs} = 1mA$?

Require a shunt in series with

$$50 = V_{ab} = (R_s + R_c) I_{fs}$$

$$\Rightarrow R_s = \frac{V_{ab}}{I_{fs}} - R_c = \frac{50}{10^{-3}} - 20 = 50,000 - 20$$


$$R_{sh} = \underline{49,980\Omega}$$

= required shunt resistance.

Ammeters + Voltmeters are never perfect




Ammeter + coil resistance

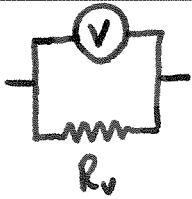

Voltmeter + finite resistance

e.g

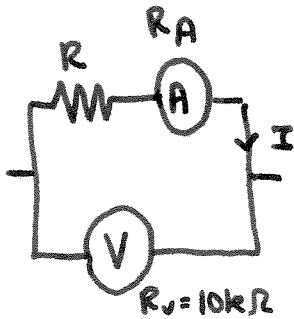

$$R_A = 2\Omega$$

$$R_v = 10k\Omega$$

$$V = 12V$$

$$I = 0.1A$$

• What is the resistance R ?

$$V = IR + IR_A \quad \Rightarrow \quad R = \frac{V}{I} - R_A = \frac{12}{0.1} - 2$$

$$= 120 - 2$$

$$= 118\Omega$$

$$• P = V_{ab}I = I^2R = 0.1(11.8) = \underline{1.18W}$$


- Ohmmeter -

When shorted - full swing

$$I_{fs} = \frac{\mathcal{E}}{R_0}$$


With finite R
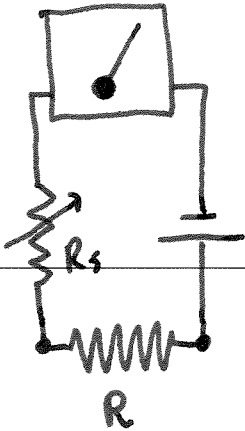
$$I = \frac{\mathcal{E}}{R_0 + R} = \frac{I_{fs}}{1 + R/R_0}$$



- Potentiometer

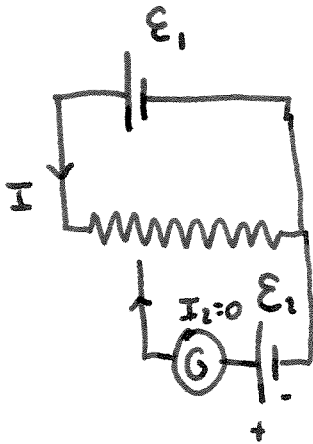Measures EMF of source without drawing any current.




$$IR_{ab} = \mathcal{E}_1$$

$$IR_{ab} = \mathcal{E}_2 \quad \text{when } I_2 = 0.$$

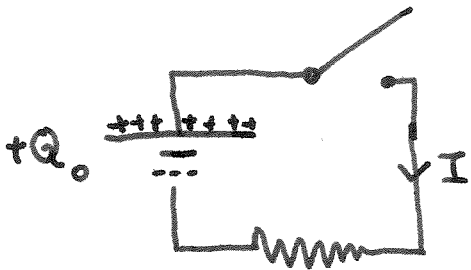26.4 R-C Circuits

When we discharge, or charge up a capacitor, we have to deal with time-dependent currents. Charge up a capacitor to $Q_0 = \epsilon_0 C$. Now discharge it



DISCHARGE

Kirchoff $\left. \begin{array}{l} \frac{Q}{C} - IR = 0 \end{array} \right\}$

$$Q = -CR \frac{dQ}{dt}$$

$$I = \frac{dQ}{dt}$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = - \int_0^t \frac{dt}{CR}$$

$$\Rightarrow \ln \frac{Q}{Q_0} = - \frac{t}{CR}$$

$$\Rightarrow \frac{Q}{Q_0} = e^{-t/CR}$$


$$Q = Q_0 e^{-t/\tau}$$

$$\underline{\tau = CR}$$


$$I = -\frac{dQ}{dt} = \frac{Q_0}{CR} e^{-t/CR} = I_0 e^{-t/CR}$$

\uparrow
 initial current.

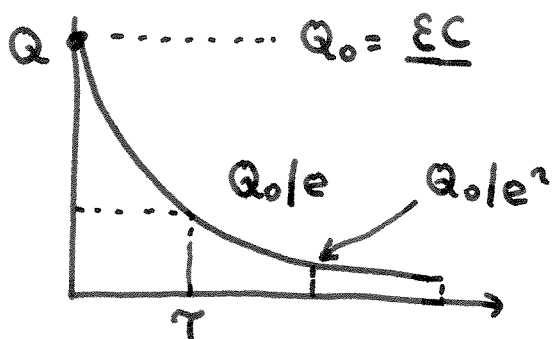e.g. $C = 2.6 \mu\text{F}$ $R = 2 \text{M}\Omega \Rightarrow \tau = \underline{\underline{5.2 \text{s}}}$.



Charging

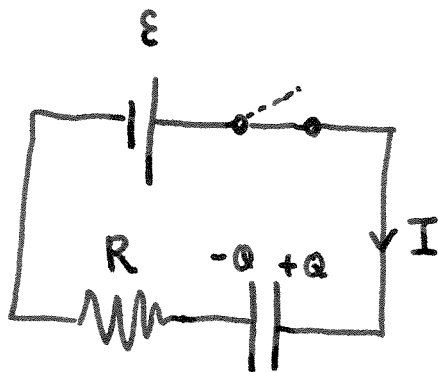

$$\epsilon - Q/C - IR = 0$$

$$\frac{dQ}{dt} = \frac{\epsilon}{R} - \frac{Q}{CR}$$

$$I = dQ/dt$$

$$I_0 = \frac{\epsilon}{R}$$

$$Q_{\text{final}} = EC.$$

$$\frac{dQ}{dt} = \frac{1}{CR} (\epsilon C - Q)$$

Soluhon :

$$\frac{dq}{CE - Q} = \frac{dt}{CR}$$

$$\int_0^Q \frac{dq'}{CE - Q'} = \frac{t}{CR}$$

||

$$\ln\left(\frac{CE}{CE - Q}\right) = \frac{t}{\tau} \quad \tau = CR$$

$$\frac{CE}{CE - Q} = e^{t/\tau}$$

$$1 - \frac{Q}{CE} = e^{-t/\tau}$$


$$\frac{Q}{CE} = 1 - e^{-t/\tau}$$

$$Q = \frac{Q_0}{CE} \left(1 - e^{-t/CR}\right)$$

$$I = \frac{dQ}{dt} = \left(\frac{E}{R}\right) e^{-t/CR}$$

$Q = Q_0(1 - e^{-t/\tau})$ $I = I_0 e^{-t/\tau}$
--


$C\varepsilon$ ← independent of R .

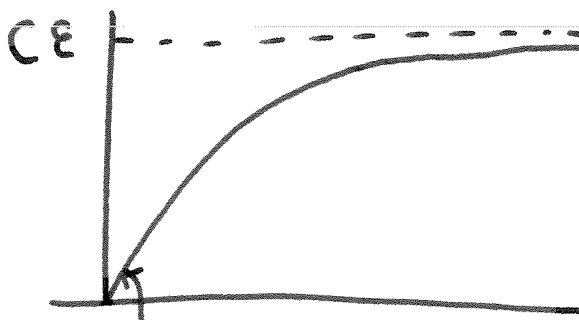

$I_0 = \frac{\varepsilon}{R}$ (independent of C)

e.g

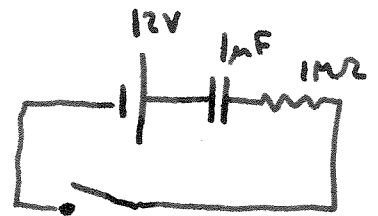Resistor with $R = 1M\Omega$ in series + $1\mu F$



with $\varepsilon = 12V$. Before switch is closed $Q=0$.

- a) What is the time constant? What is initial current I_0 ?
- b) What fraction of the initial current remains after $5s$.
- c) How long before $I/I_0 = 1/2$?

a) $\tau = CR = 10^{-6} \times 10^6 \Omega = \underline{1s}$. $I_0 = \varepsilon/R = \underline{12 \times 10^{-6} A}$

b) $I/I_0 = e^{-t/\tau} = e^{-5} = \underline{6.74 \times 10^{-3}}$

c) $I/I_0 = 1/2 = e^{-t/\tau} \Rightarrow \ln(0.5) = -t/\tau$
 $t = -\tau \ln(0.5) = \underline{6.93s}$