

# L21 MUTUAL INDUCTANCE

## +LC + LCR CIRCUITS


Today, after returning briefly to the topic of inductance, we will look at oscillatory "LC" circuits. You will see that these are the electrical analog of a weight on a spring, or a pendulum.

## 30.1 Mutual Inductance

Just as a coil has a self inductance, it can also induce an e.m.f in any other electrical coil which couples to its magnetic field. We define

$$M_{21} = \frac{N_2 \Phi_{B2}}{i_1} = \frac{N_1 \Phi_{B1}}{i_2}$$

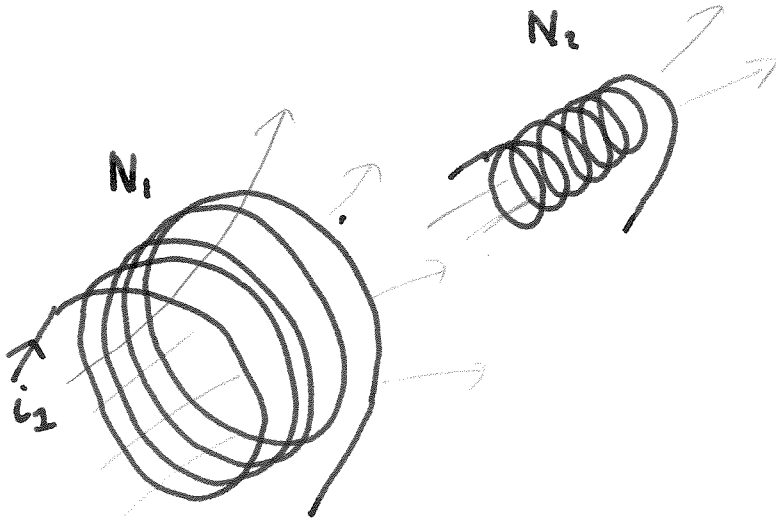as the mutual inductance between coil two and the current in coil 1.



$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{32}}{dt} = -M_{21} \frac{di_1}{dt}$$

It turns out that the mutual inductance of 1 from 2 is equal to the mutual inductance


of 2 from 1, so that  $M_{21} = M_{12} \left( = \partial^2 U_B / \partial i_1 \partial i_2 \right)$

$$M = M_{12} = M_{21}$$

$$\mathcal{E}_2 = -M \frac{di_1}{dt}$$

$$\mathcal{E}_1 = -M \frac{di_2}{dt}$$

e.g. Mutual inductance of two coils

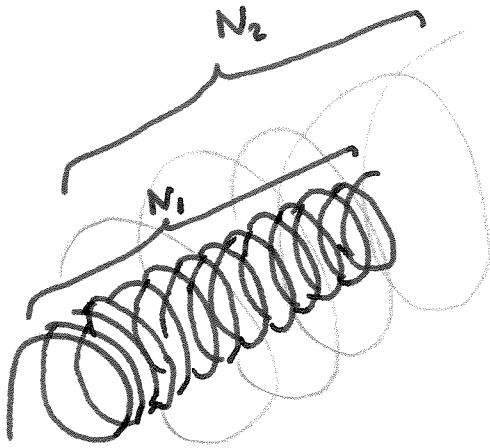

$$B_1 = \mu_0 n_1 i_1 = \mu_0 \frac{N_1}{L} i_1$$

$$M = \frac{N_2 \Phi_{B2}}{i_2} = \frac{N_2 B_1 A}{i_2} = \frac{N_2 \mu_0 N_1 A}{L} = \frac{\mu_0 N_1 N_2 A}{L}$$

e.g.  $L = 0.5 \text{ m}$ ,  $A = 10 \text{ cm}^2 = 10^{-3} \text{ m}^2$ ,  $N_1 = 1000$ ,  $N_2 = 10$

$$M = \frac{(4\pi \times 10^{-7} \text{ Wb/A}\cdot\text{m}) (10^{-3}) (1000) (10)}{0.5} = 8\pi \times 10^{-6} \text{ H} \\ \approx \underline{25 \mu\text{H}}$$




30.5 LC circuit

Suppose we take a charged capacitor with charge  $Q = CV$  and connect its plates together with a coil. Current will flow through the coil & charge will move from one plate to the other.


If there is no resistance then the total energy

$$U = \underbrace{\frac{1}{2} Li^2}_{U_B} + \underbrace{\frac{1}{2} \frac{Q^2}{C}}_{U_E}$$

will be conserved.

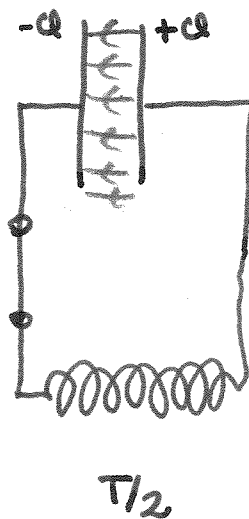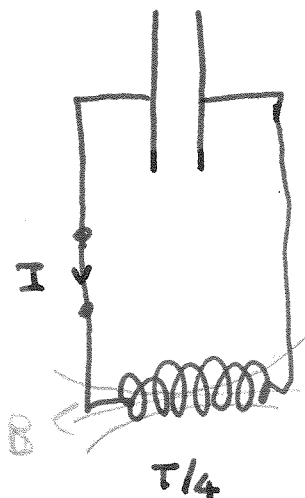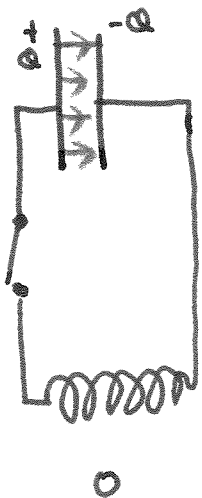

Kirchoff's law: LC circuit

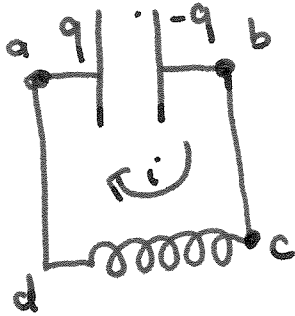

$$V_{ab} = \frac{q}{C} \quad V_{cd} = L \frac{di}{dt}$$

$$-\frac{q}{C} - L \frac{di}{dt} = 0 \Rightarrow \frac{di}{dt} + \frac{q}{LC} = 0$$

$$i = \frac{dq}{dt} \Rightarrow \frac{di}{dt} = \frac{d^2q}{dt^2}$$

$$\frac{d^2q}{dt^2} + \frac{q}{LC} = 0$$

Recall  $\frac{d^2x}{dt^2} + \left(\frac{k}{m}\right)x = 0$

$$x = A \cos[\omega t + \phi]$$

$$\frac{d^2x}{dt^2} = -\omega^2 x \Rightarrow \omega^2 = k/m, \omega = \sqrt{\frac{k}{m}}$$

Now

$$q = Q \cos(\omega t + \phi)$$


$$i = \frac{dq}{dt} = -\omega Q \sin(\omega t + \phi)$$

$$\frac{d^2q}{dt^2} = -\omega^2 q \Rightarrow c^2 = \frac{1}{Lc}$$

$$\omega = \frac{1}{\sqrt{Lc}}$$

$$f = \omega/2\pi$$

OSCILLATION  
FREQ

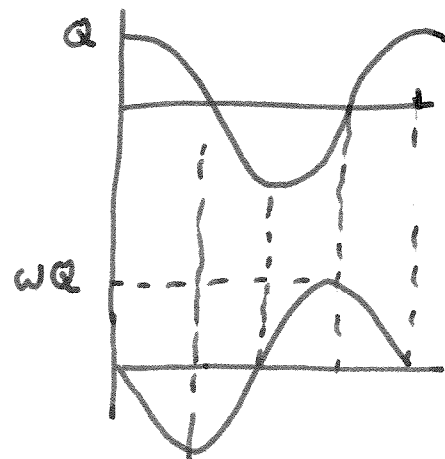

Energy conservation . Spring  $\frac{1}{2}mv^2 + \frac{kx^2}{2} = U = \frac{1}{2}kA^2$

$$v = \pm \sqrt{\frac{k}{m}} \sqrt{A^2 - x^2}$$

LC circuit

$$i = \pm \frac{1}{\sqrt{LC}} \sqrt{Q^2 - q^2}$$

Mass-Spring	LC circuit
$KE = \frac{1}{2}mv^2$ $PE = \frac{1}{2}kx^2$ $\frac{1}{2}mv^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$ $v = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$ $v_x = dx/dt$ $\omega = \sqrt{\frac{k}{m}}$ $x = A \cos(\omega t + \phi)$	$M.E = \frac{1}{2}Li^2$ $E.E = q^2/2c$ $\frac{1}{2}Li^2 + \frac{1}{2}\frac{q^2}{c} = \frac{1}{2}\frac{Q^2}{c}$ $i = \pm \frac{1}{\sqrt{LC}} \sqrt{Q^2 - q^2}$ $i = dq/dt$ $\omega = \frac{1}{\sqrt{LC}}$ $q = Q \cos(\omega t + \phi)$



$$\text{Energy} = \frac{1}{2} Li^2 + \frac{q^2}{2c} = U = \frac{Q^2}{2c}$$


$$i^2 = \frac{1}{L} \left( \frac{Q^2 - q^2}{c} \right) = \frac{1}{Lc} (Q^2 - q^2)$$

$$i = \frac{1}{\sqrt{Lc}} \sqrt{Q^2 - q^2}$$

e.g.  $25\text{ }\mu\text{F}$  charged up by  $300\text{V}$  power supply,  
connected to a  $10\text{mH}$  inductor.

a) Find  $f$  &  $T$

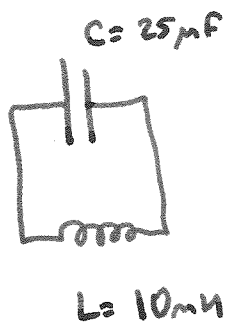b)  $q(t)$   $i(t)$  @  $t = 1.2\text{ms}$



$$a) \quad \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 25 \times 10^{-6}}} = \frac{1}{5 \times 10^{-4}} \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = \frac{2000}{2\pi} = \underline{320\text{Hz}}$$

$$T = \frac{1}{f} = \frac{1}{320\text{Hz}} = 3.1 \times 10^{-3} = \underline{3.1\text{ms}}$$

$$b) \quad Q = CV = 25 \times 10^{-6} \times 3 \times 10^2 = 7.5 \times 10^{-3} \text{ C} = \underline{7.5\text{mC}}$$

$$q(t) = 7.5 \times 10^{-3} \cos(2 \times 10^3 t)$$


$$i = -7.5 \times 10^{-3} \times 2 \times 10^3 \sin(2000t) = -15 \sin(2000t)$$

$$t = 1.2 \mu\text{s}$$


$$q(t) = 7.5 \times 10^{-3} \cos(2.4) \\ = \underline{\underline{-5.5 \times 10^{-3} \text{ C}}}$$

$$i(t) = -15 \sin(2.4) = \underline{\underline{-10 \text{ A}}}$$

## 30.6 Damped oscillations: LCR circuit

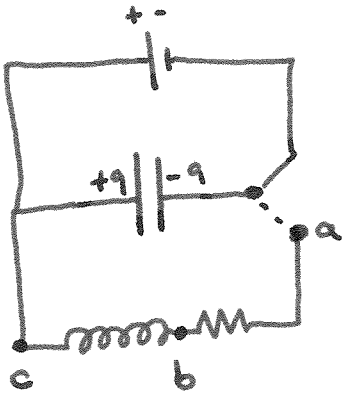


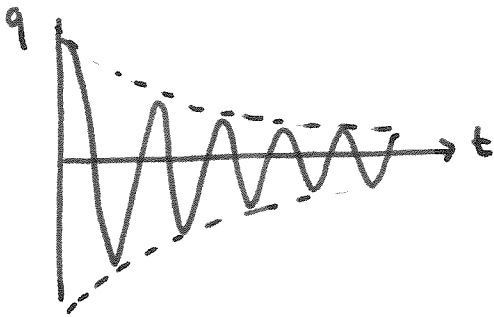Resistance  $\sim$  friction  
(i.e. losses in resistor)




a) underdamped.  $R < 2\sqrt{\frac{L}{C}}$ .

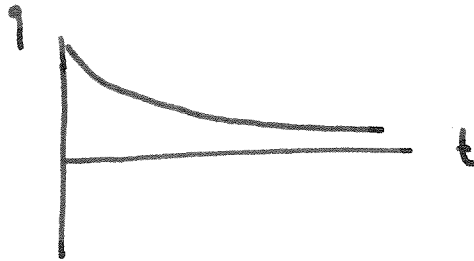
b) Critically damped.  
 $R = 2\sqrt{\frac{L}{C}}$



c) Overdamped

$R > 2\sqrt{\frac{L}{C}}$ .

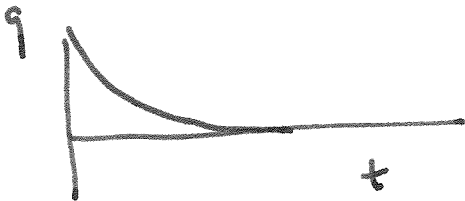

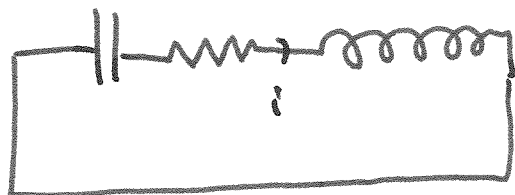

$$-\frac{q}{C} - iR - L \frac{di}{dt} = 0$$

$$\frac{d^2 q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0$$

c.f. damped  
harmonic  
oscillator.

$R=0 \Rightarrow \equiv LC$  circuit.

general soln.  $(R < 2\sqrt{LC})$

$$q = Q e^{-R/2L t} \cos \left( \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} t + \phi \right)$$

$$\tilde{\omega} = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \rightarrow 0 \text{ as } R \downarrow$$

p.s note  $\tilde{\omega} = \sqrt{\omega_0^2 - \frac{1}{(2\tau)^2}}$

e.g a) What  $R$  is required so that

$$\omega = \omega_0/2 ?$$

$$\omega = \sqrt{\omega_0^2 - \frac{R^2}{4L^2}} = \frac{\omega_0}{2}$$

$$\omega_0^2 - R^2/4L^2 = \omega_0^2/4$$

$$(R^2/4L^2) = 3\omega_0^2/4$$

$$R^2 = 3\omega_0^2 L^2 = \frac{3L}{C}$$

$$R = \sqrt{\frac{3L}{C}}$$

b) If  $f_0 = 4 \text{ MHz}$  &  $L/R = 1 \mu\text{s}$  calculate

$f$ .

$$\begin{aligned} f &= 2\pi \sqrt{\omega_0^2 - (1/2\tau)^2} = \sqrt{f_0^2 - \left(\frac{2\pi}{2\tau}\right)^2} \\ &= \sqrt{(4 \times 10^6)^2 - \left(\frac{3.14}{10^{-6}}\right)^2} \\ &= 10^6 \times \sqrt{6.13} = 2.47 \times 10^6 \text{ Hz} \\ &= \underline{\underline{247 \text{ MHz}}} \end{aligned}$$