

Power in our National grid comes in the form of an alternating current or "a.c" power supply.

Many electrical devices depend on this a.c supply

& it is vital that we understand a.c. circuitry.

We'll see that we need to extend Ohm's law to include the concept of a frequency dependent resistance or "reactance" X . We will write

$$V = I X$$

(X depends on frequency).

Where V & I are the amplitudes of the voltage & current.

31.1 Alternating Current

(a) Voltage



a.c source

$$v = V \cos \omega t$$

instantaneous voltage

AMPLITUDE

angular frequency
 $\omega = 2\pi f$
 $f = 60 \text{ Hz}$ N. America
 $= 50 \text{ Hz}$ Europe/Asia.


b) Current

$$i = I \cos \omega t$$

instantaneous current


amplitude

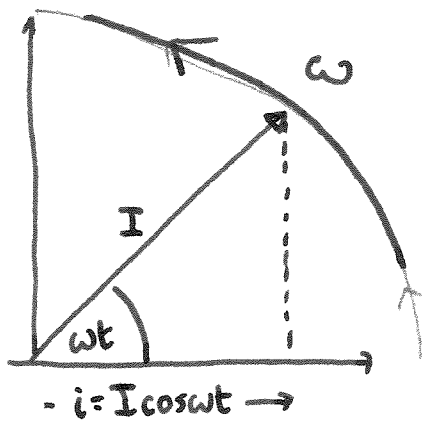b) Phasors : a convenient way to
 represent sinusoidally varying
 quantities.





$$i = I \cos \omega t$$

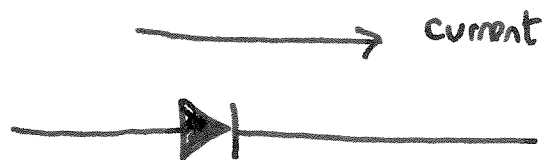We can measure an ac current in various ways —
 with an oscilloscope — also by "rectifying" the
 current using a diode.




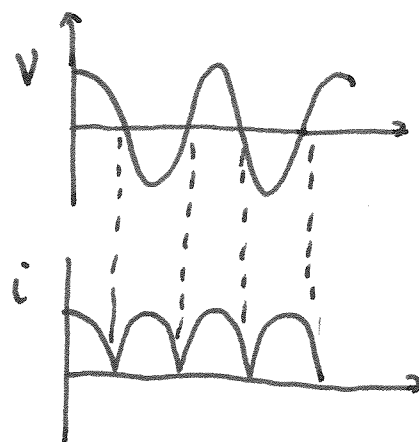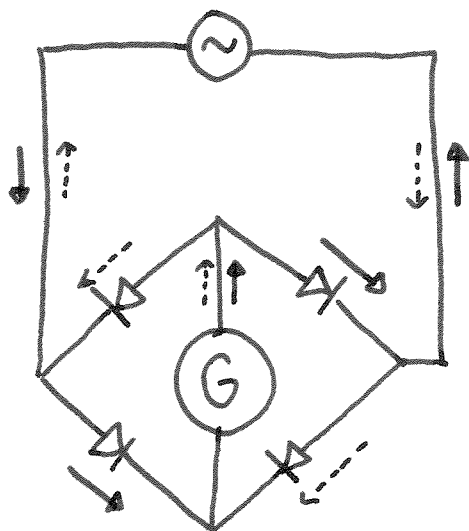A diode only transmits a current in the direction of the arrow.



Current only flows one way through the galvanometer.

$$i_{\text{rav}} = \overline{i_{\text{rectified}}} = \frac{\int_0^{2\pi/\omega} I |\cos \omega t| dt}{\left(\frac{2\pi}{\omega}\right)}$$

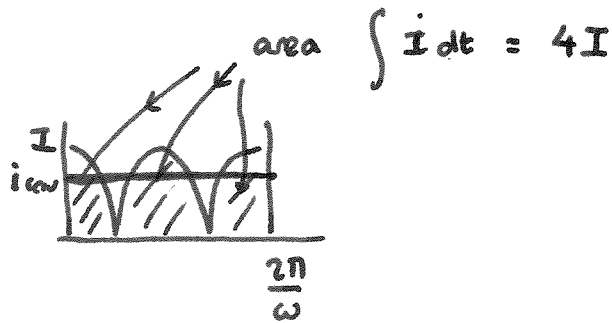

$$= \frac{4 \int_0^{\pi/2\omega} I \cos \omega t dt}{\left(\frac{2\pi}{\omega}\right)} = \frac{4I}{\frac{2\pi}{\omega}}$$

$$i_{\text{rav}} = \left(\frac{2}{\pi}\right) I$$

More useful concept is the r.m.s or "root-mean-square current"

$$I_{\text{rms}} = \sqrt{i^2}$$

$$i^2 = I^2 \cos^2 \omega t$$

Now remember that

$$\cos^2 A = \frac{1}{2} (1 + \cos 2A)$$

50

$$i^2 = I^2 \left(\frac{1}{2} + \frac{1}{2} \cos 2A \right)$$

average = 0.

$$\overline{i^2} = \frac{I^2}{2}$$

$$i_{\text{rms}} = \frac{I}{\sqrt{2}}$$

root-mean squared current.

$$V_{\text{rms}} = \frac{V}{\sqrt{2}}$$

root-mean squared voltage.

Note that when we say we have a 120V a.c. supply
 we mean $V_{\text{rms}} = 120\text{V}$, i.e. $V = \sqrt{2} \times 120\text{V} = \underline{170\text{V}}$

e.g. Computer draws 2.7A from a 120V 60Hz line.

a) Average current

b) Average of the square of the current

c) Current amplitude.



a) $i_{rms} = 2.7 A$

• Average current = $\overline{I} = 0$.

b) $i_{rms} = 2.7 A$

c) $I = \sqrt{2} \times 2.7 A = 3.8 A$.

31.2 "REACTANCE"

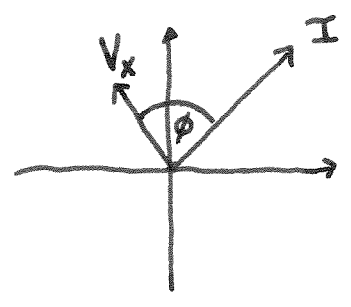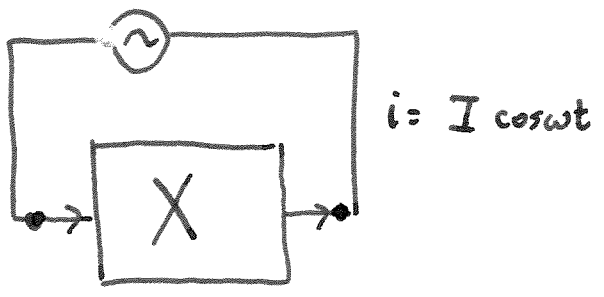

$i = I \cos \omega t$


$$V_x = X I \cos(\omega t + \phi_x)$$

voltage amplitude
↓

$$V_x = I X$$
↑
reactance

X is called the "reactance" - it is a generalization of the concept of resistance.

e.g Resistor

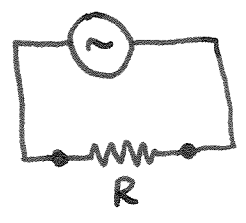



$$V_R = iR = (IR) \cos \omega t$$

$$= V_R \cos \omega t$$

$V_R = IR$



$X = R$

current + voltage
IN PHASE

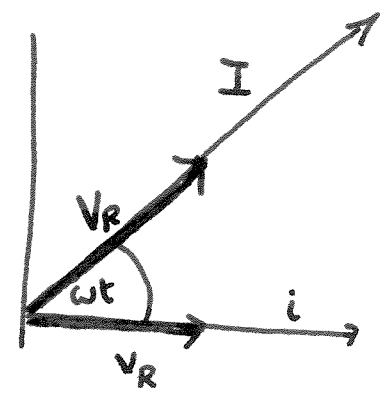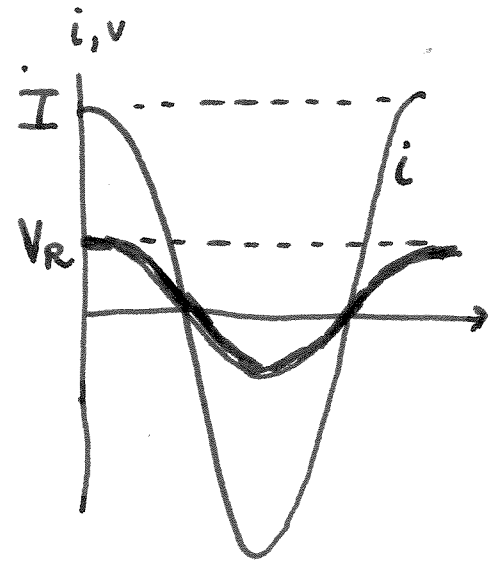

$$X_R = R$$
$$\phi_R = 0^\circ$$

(b) Inductor

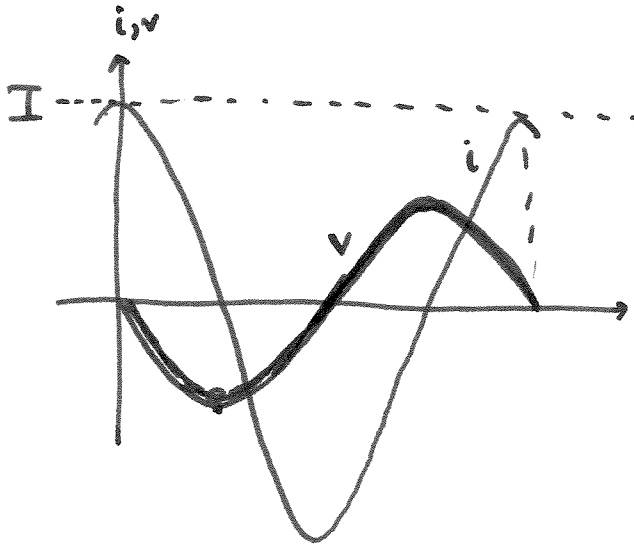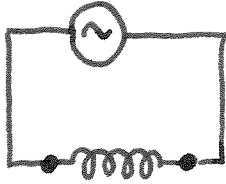


$$v = L \frac{di}{dt}$$

$$= L \frac{d}{dt} I \cos \omega t$$

$$= -L I \omega \sin \omega t$$
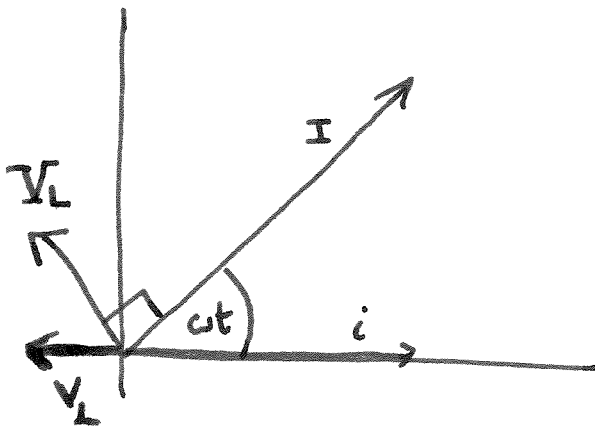
$$v = \omega L I \cos(\omega t + 90^\circ)$$



$$\begin{cases} X_L = \omega L \\ \phi_L = 90^\circ \end{cases}$$

$$V_L = \omega L I$$

The amplitude of the voltage across the inductor

is $(\omega L) \times I$; the voltage "leads" the current by $\frac{1}{4}$ cycle.

e.g. Require $I_L = 250 \mu\text{A}$ in an inductor in a radio receiver when $V_L = 3.60 \text{V}$ & $f = 1.6 \text{MHz}$

a) What inductive reactance X_L is needed? What L ?

b) If the voltage amplitude is constant, what will the current amplitude be at 16MHz & 160MHz ?

$$a) \quad V_L = I X_L \Rightarrow X_L = \frac{V_L}{I_L} = \frac{3.6 \text{V}}{250 \times 10^{-6} \text{A}}$$

$$= 1.44 \times 10^4 \Omega$$



$$= \underline{14.4 \text{k}\Omega}$$

$$\omega L = X_L \Rightarrow L = \frac{1.44 \times 10^4}{2\pi \times 1.6 \times 10^6} =$$

$$b) \quad I_L = \frac{V_L}{X_L} = \frac{V_L}{\omega L} \quad \left. \begin{array}{l} \\ \end{array} \right\} \underline{1.43 \times 10^{-3} \text{H} = 1.43 \text{mH}}$$

$$I_L(16 \text{MHz}) = \frac{3.60 \text{V}}{2 \times \pi \times (16 \times 10^6) \times 1.43 \times 10^{-3}} = \frac{25 \times 10^{-6} \text{A}}{25 \mu\text{A}}$$

$$I_L(160 \text{MHz}) = 2.5 \mu\text{A}$$

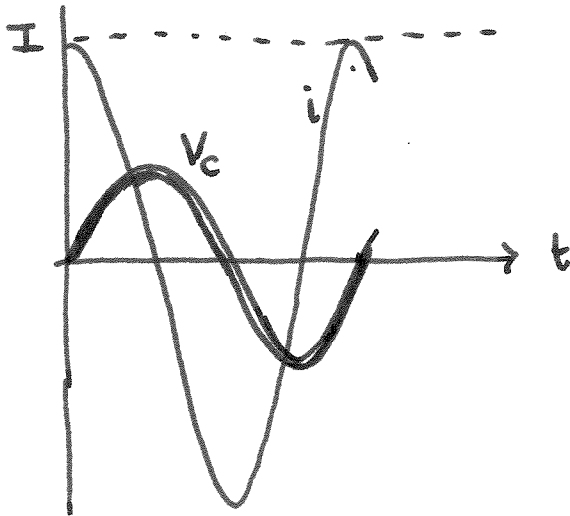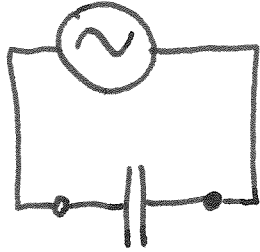c) Capacitor

$$i = \frac{dq}{dt} = I \cos \omega t$$

$$q = \frac{I}{\omega} \sin \omega t$$

$$v = \frac{q}{C} = \frac{I}{\omega C} \sin \omega t$$


$$v_c = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$$

$$V_c = \frac{1}{\omega C} I_c$$

$$X_c = \frac{1}{\omega C}$$

$$\phi_c = -90^\circ$$

$$V_c = I_c X_c$$

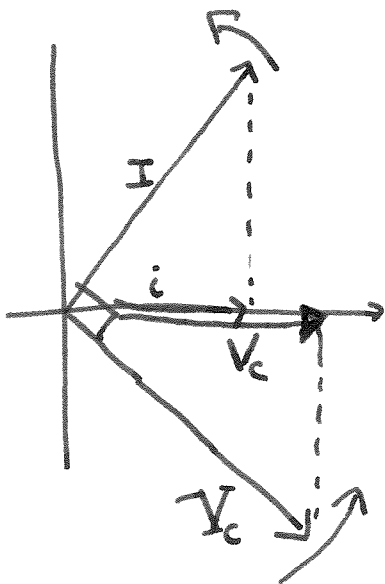


$$c) \quad V_c = V_c \cos(\omega t - \pi/2)$$

$$V_c = IX_c = 6 \times 10^{-3} \times 80 = 0.48 \text{ V}$$


$$V_c = 0.48 \text{ V} \cos((2500 \text{ rad/s})t - \pi/2 \text{ rad}).$$

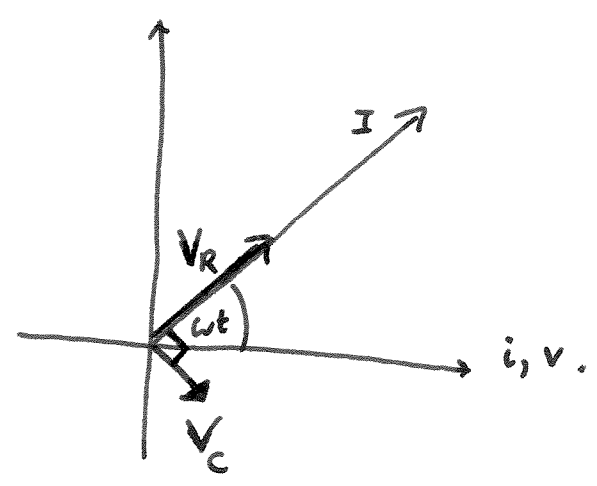n.b converted 90° to radians since argument of cosine is given in radians.



Summary

Circuit element	Amplitude relation	Circuit quantity	ϕ
Resistor	$V_R = IR$	R	0
Inductor	$V_L = IX_L$	$X_L = \omega L$	90°
Capacitor.	$V_C = IX_C$	$X_C = 1/\omega C$	-90°

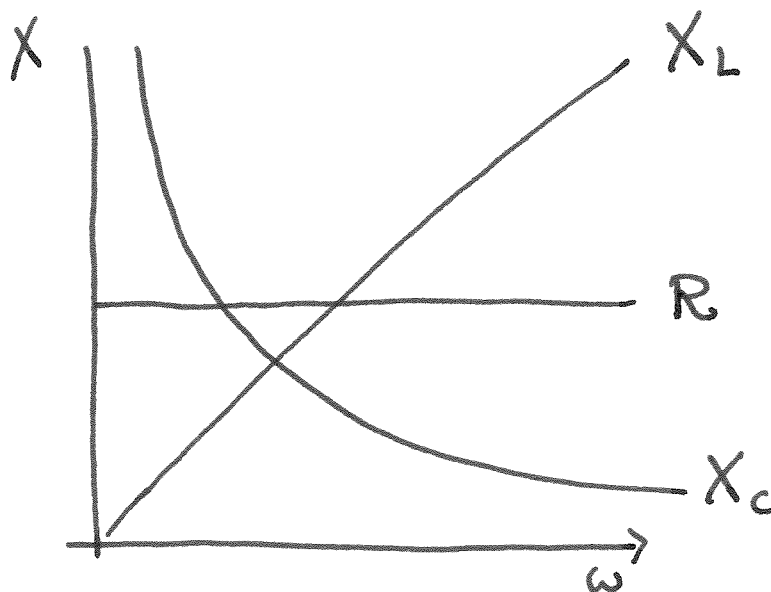

$$V = IX$$

$X_C \rightarrow \infty$ at low frequencies (high pass)

$X_L \rightarrow \infty$ at high frequencies (low pass)