

L23

LCR Circuits

Last lecture, we examined the response of resistors, capacitors & inductors to an a.c. voltage. Whereas the voltage & current through a resistor are in phase & given by

$$V_R = IR \quad \phi_R = 0 \quad \text{---} \text{---} \text{---}$$


the voltage & current through an inductor are 90° out-of phase

$$V_L = IX_L \quad \phi_L = 90^\circ$$


where $X_L = \omega L$ is the "reactance", whereas for a capacitor

$$V_C = IX_C \quad \phi_C = -90^\circ$$

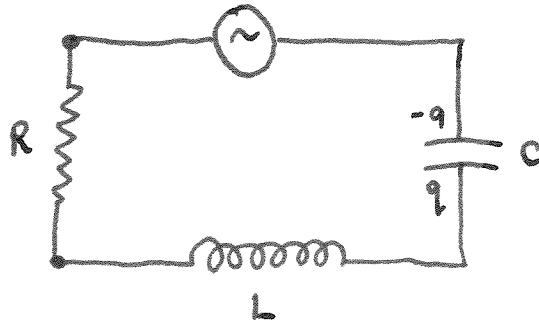& $X_C = 1/\omega C$. Now we wish to examine the behavior of a series combination of all three - the LCR circuit.



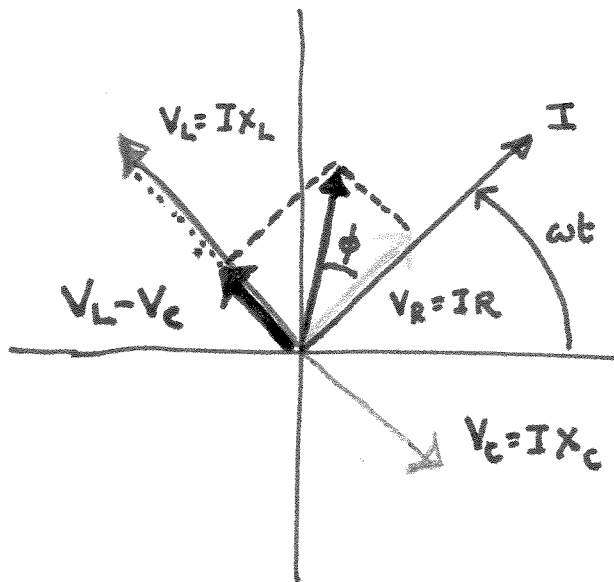To represent the voltages through each element we will use "phasors". Lets assume $X_L > X_C$.



The voltage contains two parts, an "in phase" part $V_R = IR$ & a reactive part $V_L - V_C = I(X_L - X_C)$.

The resultant has magnitude

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

or

$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

We define

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

as the impedance of the L-R-C circuit, so that

$$\boxed{V = IZ}$$

Written out in full

$$Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

Now the voltage leads the current with a phase angle ϕ

where

$$\tan\phi = \frac{V_L - V_C}{V_R} = \frac{I(X_L - X_C)}{IR} = \frac{X_L - X_C}{R}$$

or

$$\tan\phi = \frac{\omega L - 1/\omega C}{R}$$

The full expression for the current is then


$$i = I \cos(\omega t + \phi)$$

Note that

$$V_{\text{rms}} = \frac{V}{\sqrt{2}} = \frac{I Z}{\sqrt{2}} = i_{\text{rms}} Z$$

This describes the steady-state. When the circuit is first connected there will in general be "transient" responses which die out to reveal the above steady state oscillation.

e.g

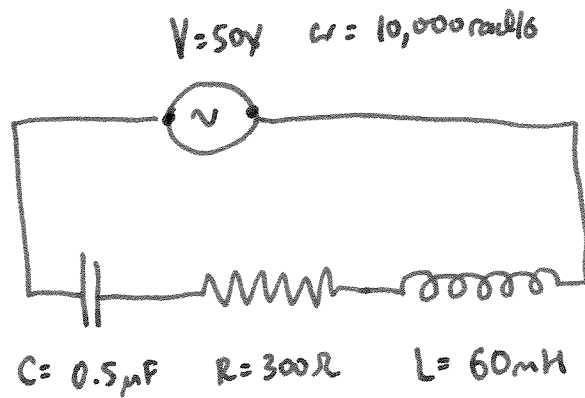

$$X_C = \frac{1}{10^4 \times 0.5 \times 10^{-6}} = 200 \Omega$$

$$X_L = 10^4 \times 60 \times 10^{-3} = 600 \Omega$$



$$Z = \sqrt{(300)^2 + (600 - 200)^2} = 500 \Omega$$

$$I = \frac{V}{Z} = \frac{50V}{500 \Omega} = 0.1 A$$

$$\tan \phi = \frac{X_L - X_C}{R} = \frac{400 \Omega}{300 \Omega} = 1.25$$

$$\phi = 53^\circ$$
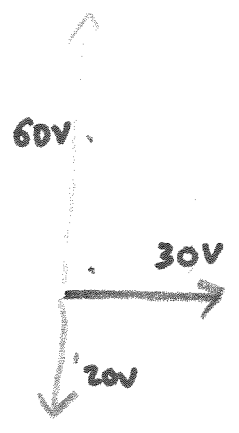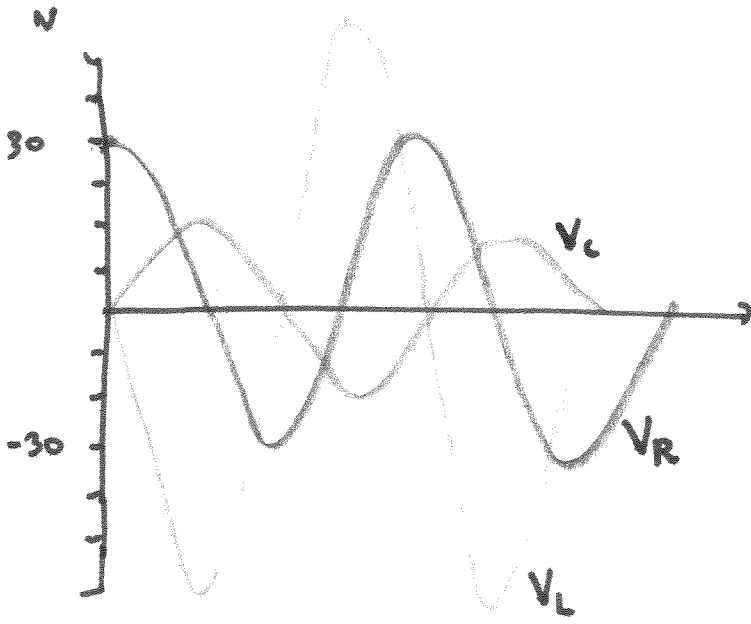
$$V_R = IR = 30V \quad V_L = IX_L = 60V \quad V_C = IX_C = 20V$$



$$p = vi$$

Pure resistance $v = V \cos \omega t$, $i = I \cos \omega t$

$$p = VI \cos^2 \omega t$$

$$P_{av} = \frac{VI}{2} = V_{rms} I_{rms}$$

$$P_{av} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$


More generally

$$\begin{aligned} vi &= [V \cos(\omega t + \phi)] I \cos \omega t \\ &= [V \cos \omega t \cos \phi - V \sin \omega t \sin \phi] I \cos \omega t \end{aligned}$$

$$v_i = VI \cos\phi \underbrace{\cos^2 \omega t}_{\text{average} = \frac{1}{2}} - VI \sin\phi \underbrace{\cos \omega t \sin \omega t}_{= \frac{1}{2} \sin 2\omega t \text{ average} = 0.}$$

$$P_{av} = \frac{1}{2} VI \cos\phi$$

$$P_{av} = V_{rms} i_{rms} \cos\phi$$


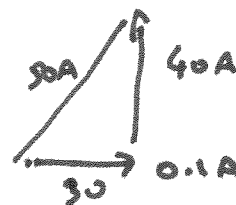


e.g. earlier example. $I = 0.1A$ $V_{rms} = 50V$. $\cos\phi = 3/5$.

$$P_{av} = \frac{1}{2} 50 \times 0.1 \times \frac{3}{5} = \underline{\underline{1.5W}}$$

31.5 Resonance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

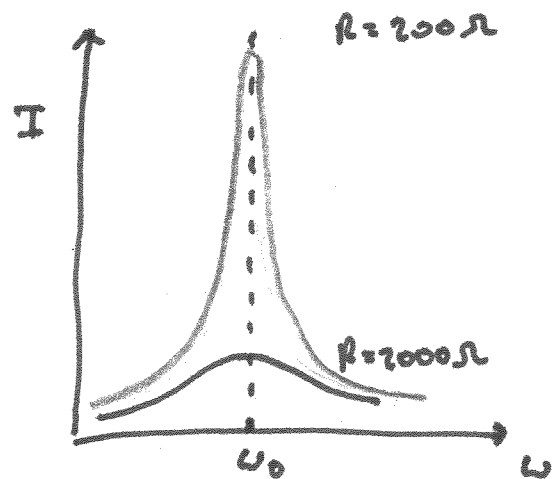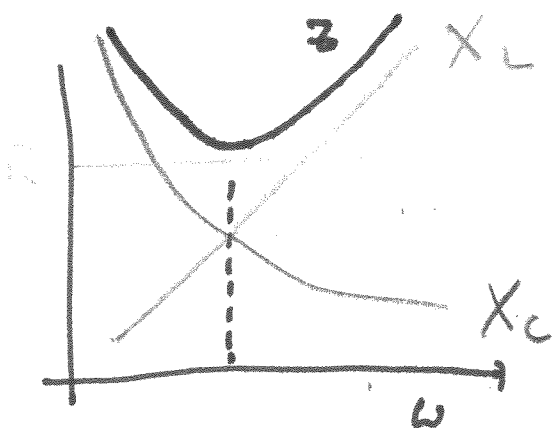


Z is minimum when $X_L = X_C$, $\omega = \omega_0$

$$\omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

This is the natural oscillation frequency.

$$I = V/Z(\omega)$$

e.g.

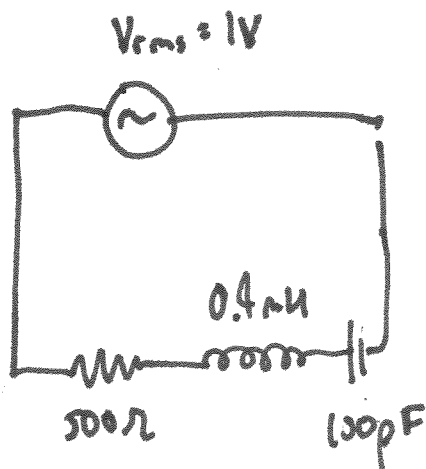

$$a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.4 \times 10^{-3} \times 100 \times 10^{-12}}}$$

$$= 5 \times 10^6 \text{ rad/s.}$$

$$f = \omega_0 / 2\pi = 8 \times 10^5 = 800 \text{ kHz}$$

$$b) \quad X_C = \frac{1}{\omega_0 (100 \times 10^{-12})} = \frac{1}{5 \times 10^6 \times 10^{-10}} = 2000 \Omega$$

$$X_L = 5 \times 10^6 \times 0.4 \times 10^{-3} = 2000 \Omega$$


$$Z = R = 500 \Omega$$

$$c) \quad V_{rms} = 1V \quad I_{rms} = \frac{V_{rms}}{Z} = \frac{1V}{500\Omega} = 2mA$$

31.6

TRANSFORMERS

23.12

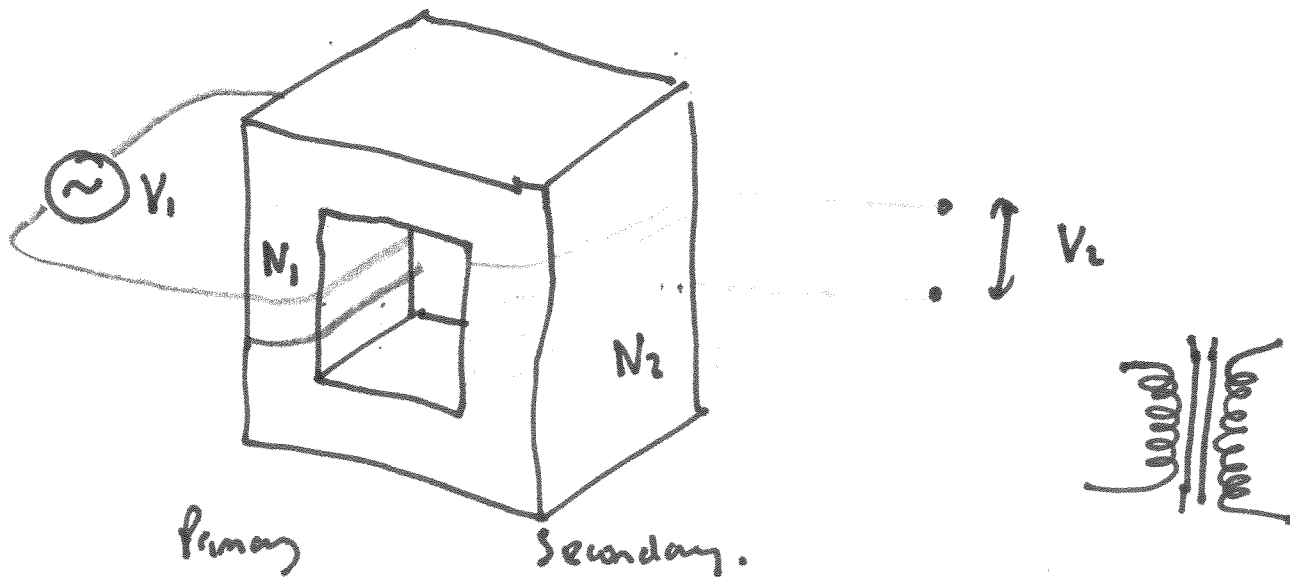

$$\mathcal{E}_1 = -N_1 \frac{d\phi_B}{dt}$$

$$\mathcal{E}_2 = -N_2 \frac{d\phi_B}{dt}$$

$$\frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{N_2}{N_1} \Rightarrow$$

$$\boxed{\frac{V_2}{V_1} = \frac{N_2}{N_1}}$$

$$V_1 I_1 = V_2 I_2$$

(energy conservation).