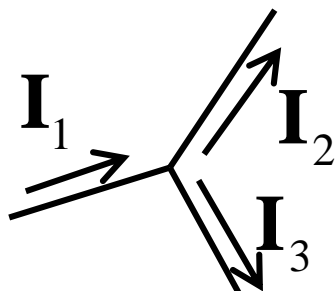



$$\mathbf{V} = \mathbf{I} \mathbf{R} \quad \mathbf{R} = \rho \left[\frac{\mathbf{L}}{\mathbf{A}} \right]$$

Kirchhoff's Laws

$$\sum_{\text{junc}} \mathbf{I}_j = 0$$



$$\sum_{\text{loop}} \mathbf{V}_j = 0$$

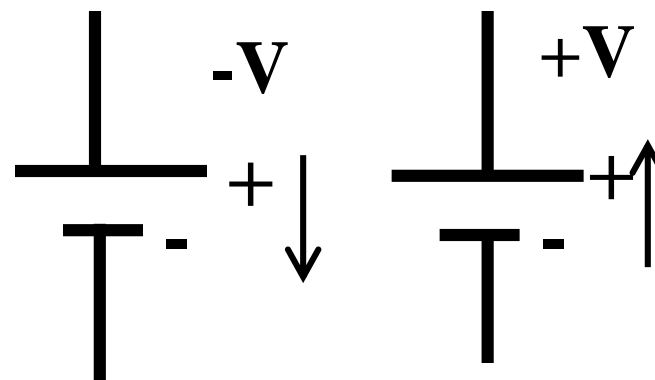


$$\mathbf{P} = \mathbf{I} \mathbf{V} = \mathbf{I}^2 \mathbf{R} = \frac{\mathbf{V}^2}{\mathbf{R}}$$

$$\mathbf{R}_{\text{eff}} = \mathbf{R}_1 + \mathbf{R}_2$$


$$\frac{1}{\mathbf{C}_{\text{eff}}} = \frac{1}{\mathbf{C}_1} + \frac{1}{\mathbf{C}_2}$$

$$\frac{1}{\mathbf{R}_{\text{eff}}} = \frac{1}{\mathbf{R}_1} + \frac{1}{\mathbf{R}_2}$$
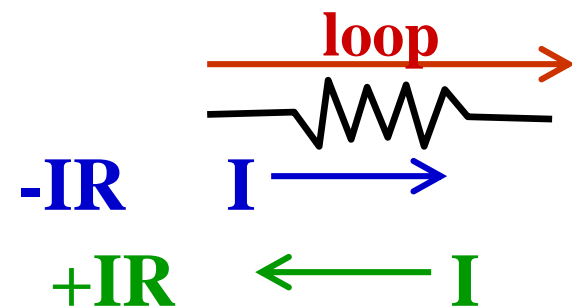
$$\mathbf{C}_{\text{eff}} = \mathbf{C}_1 + \mathbf{C}_2$$



Charges in motion

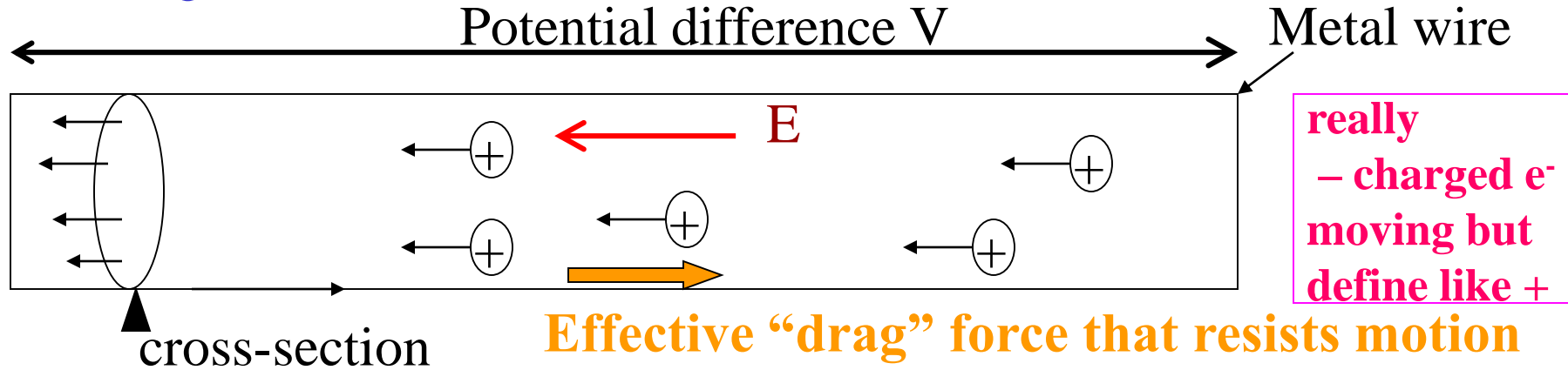

charge Δq flows through in Δt

$$I = \frac{\Delta q}{\Delta t}$$

current = $\frac{\text{coulombs}}{\text{sec}}$ = ampere




Electric Potential Source



Battery – dry cell 1.5V

Hg cell 1.35V

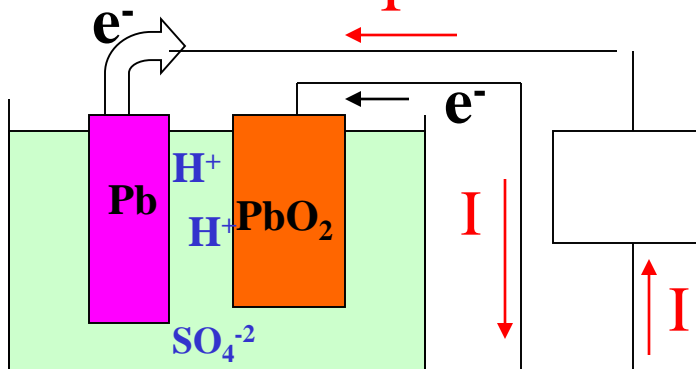

Chemical energy \longrightarrow electrical energy

$$EL = \left[\frac{m}{n q \tau} \right] \left[\frac{L}{A} \right] I$$

$$V = \rho \left[\frac{L}{A} \right] I$$

electrical resistivity

$$\rho = \left[\frac{m}{n q \tau} \right]$$

material's reluctance
to carry current

Ohm's
Law

$$V = R I$$

applied
voltage


resistance

current

$$R = \rho \left[\frac{L}{A} \right]$$

material
property


geometrical
factor

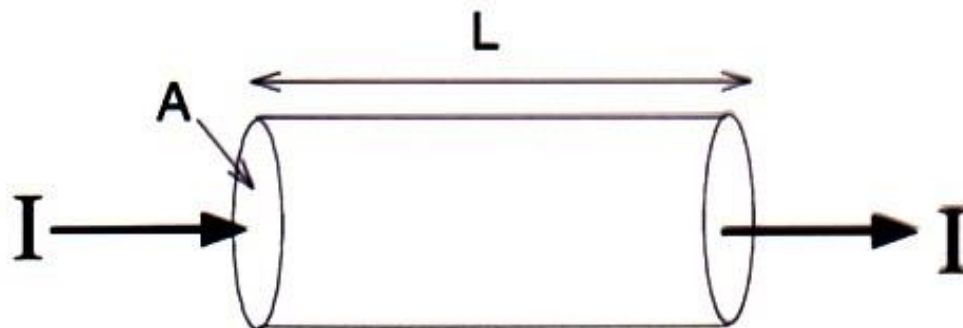

Example: $10\ \Omega$ resistor

$$V = IR = I(10)$$

$$V = 10 I \text{ theory.}$$


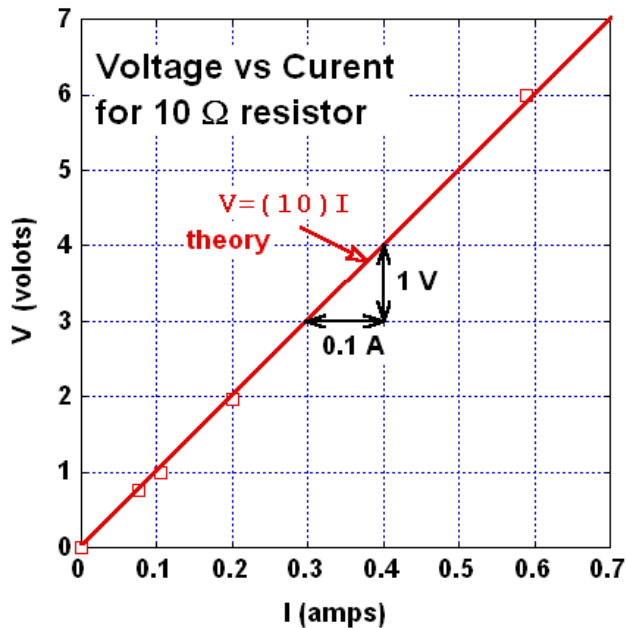


units

$$\Omega = \frac{V}{A} = \frac{\frac{J}{C}}{\frac{C}{sec}} = \frac{J \cdot sec}{C^2} = \frac{\left(kg \frac{m^2}{sec^2} \right) sec}{C^2} = \frac{kg \cdot m^2}{sec \cdot C^2}$$

3-3


Represent + battery with picture

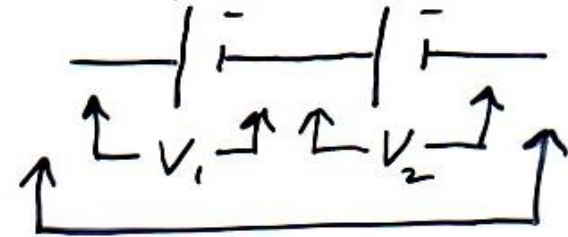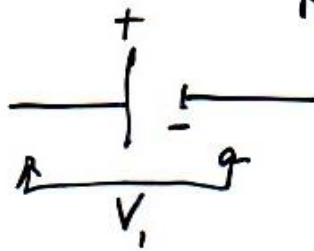

$$V = V_1 + V_2$$

add batteries to make larger Voltage

Ohm's Law

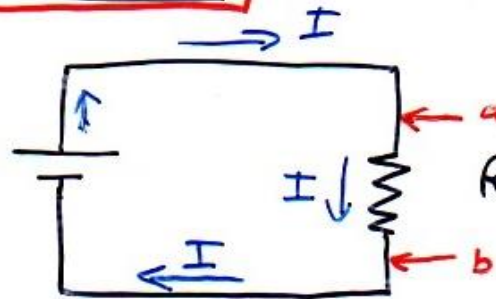


$R = \text{resistance (ohms, } \Omega \text{)}$
resistor

$$V_{ab} = I R$$

Electrical Measurements

“Amp” meter (very little resistance)

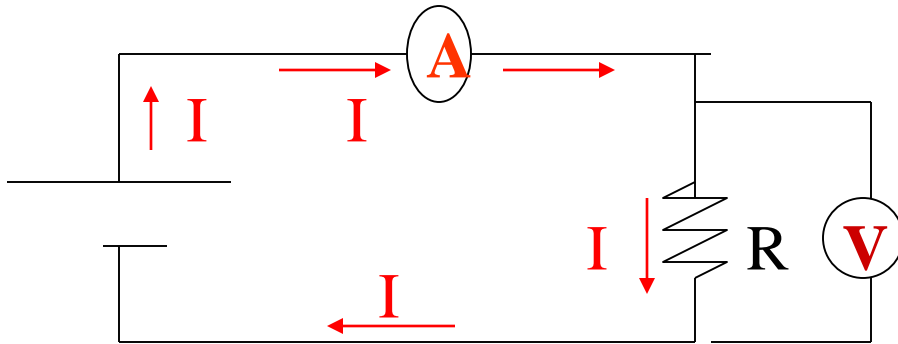


**Volt meter (very large resistance)
(draws ~NO current.)**

DC (direct current) multi-meters measures volts & amps.

Don't make a mistake on settings! [especially don't try to measure V on amp setting]

Many meters also measures R (Ω)

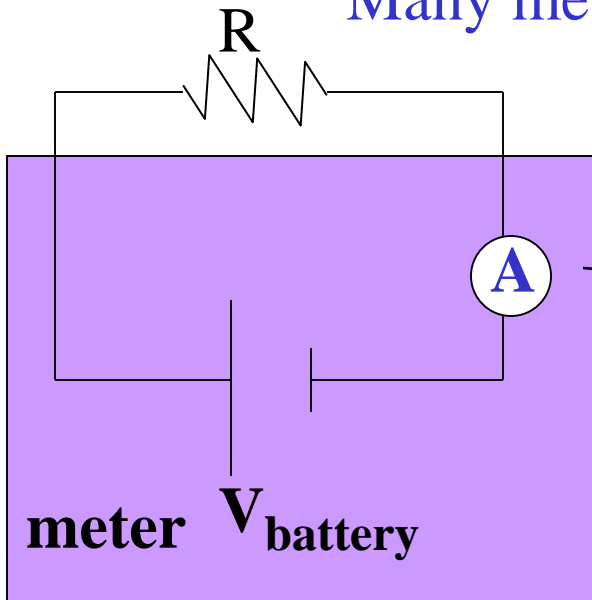


$$V_{\text{battery}} = IR$$

Measures I for known V_{bat} so..

$$R = \frac{V_{\text{bat}}}{I}$$

Power dissipated to heat in resistor

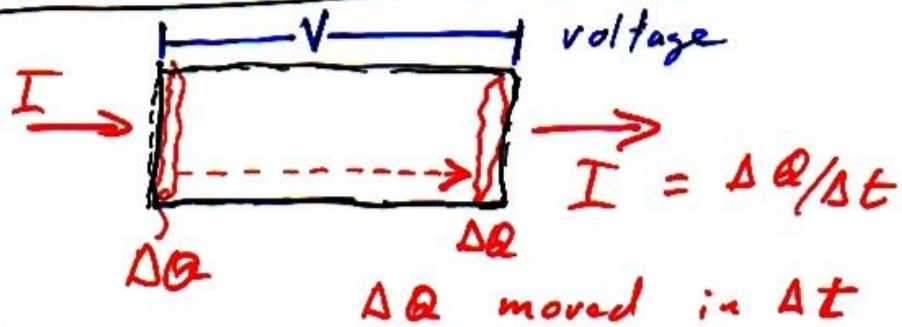

work done in moving ΔQ across V

$$\Delta W \equiv \Delta Q V$$

(this work done in Δt)


power $P \equiv \frac{\Delta W}{\Delta t} = \frac{\Delta Q}{\Delta t} V \Rightarrow P = I V$

work/time

$(J/sec) = \text{watts} = W$

but $V = IR$ so $P = I (IR) \Rightarrow I^2 R = P$

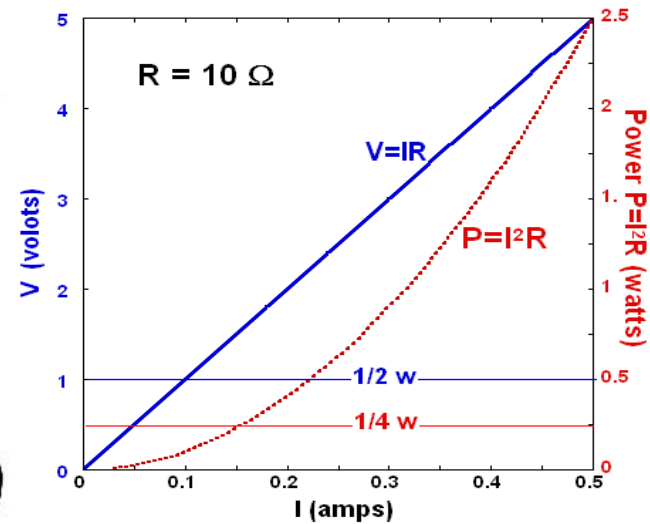also $I = \frac{V}{R}$ so $P = \left(\frac{V}{R}\right) V \Rightarrow \frac{V^2}{R} = P$




Units of power

$$P = IV$$

$$A V = \left(\frac{C}{sec} \right) \left(\frac{J}{C} \right) = \frac{J}{sec}$$

=watts

Power Example


 10Ω $\left[\frac{1}{2} \text{ W resistor} \right]$
 Limit \uparrow where it's OK

$$P = I^2 R$$

Limit \swarrow

$$0.5 \text{ (W)} = I^2 (10 \Omega)$$

$$I^2 = 0.05 \quad \left[\frac{\text{W}}{\Omega} \right]$$

$$I = \sqrt{0.05} \sqrt{\left[\frac{\text{J}}{\frac{\text{V}}{\text{A}} \text{ s}} \right]} \quad \left[\frac{\text{W}}{\Omega} \right]$$

$$I_{\text{limit}} \approx 0.22 \sqrt{\frac{\text{J}}{\frac{\text{V}}{\text{A}} \text{ s} \frac{\text{V}}{\text{A}} \frac{1}{\text{s}}}} \quad \left[\frac{\text{W}}{\Omega} \right]$$

$$I_{\text{limit}} \approx 0.22 \left(\frac{\text{C}}{\text{s}} \right) \text{ A}$$

$$\text{or } P = \frac{V^2}{R}$$

$$P = \frac{V^2}{10} \left(\frac{1}{\Omega} \right)$$

$$\text{limit} \quad 0.5 \text{ W} = \frac{V^2}{10} \left(\frac{1}{\Omega} \right) \quad V = IR$$

$$5 \text{ (W } \Omega) = V^2$$

$$\downarrow$$

$$\left(\frac{\text{J}}{\text{s}} \frac{\text{V}}{\text{A}} \right)$$

$$\downarrow$$

$$\left(\frac{\text{J}}{\text{s}} \frac{\text{V}}{\text{A}} \frac{\text{A}}{\text{V}} \right)$$


$$2.2 \frac{\text{J}}{\text{C}} = V$$

$$2.2 \text{ (V)} = V$$

volts


Circuit Analysis Kirchhoff's Laws

Conservation of current charge

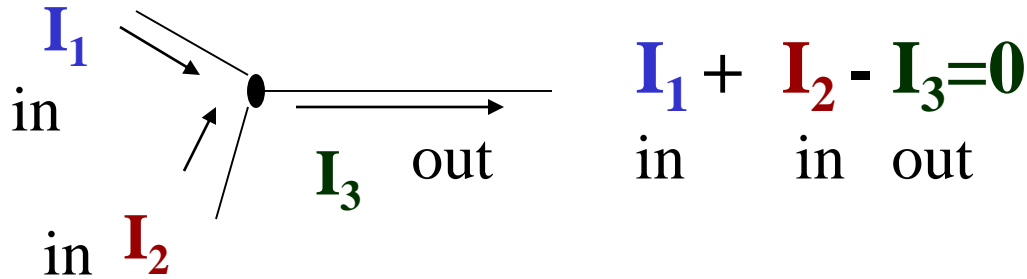


The sum of the currents into any junction must equal zero.
(charge does not build up). (+=in -=out)

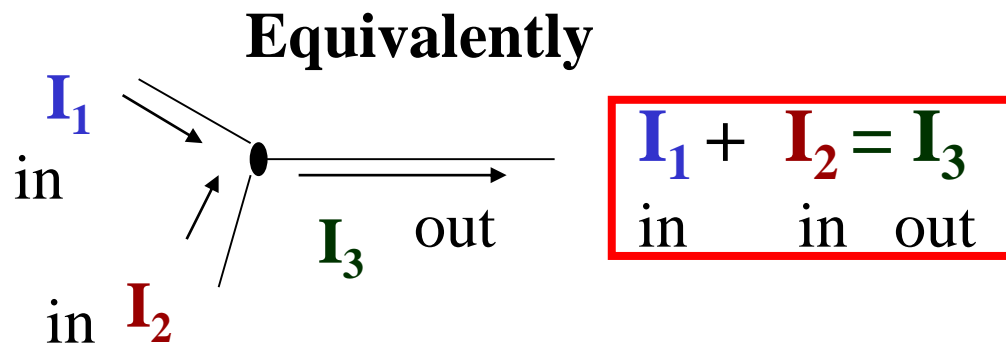You can choose any direction for I, just stay with your choice throughout.



Electric potential energy conservation

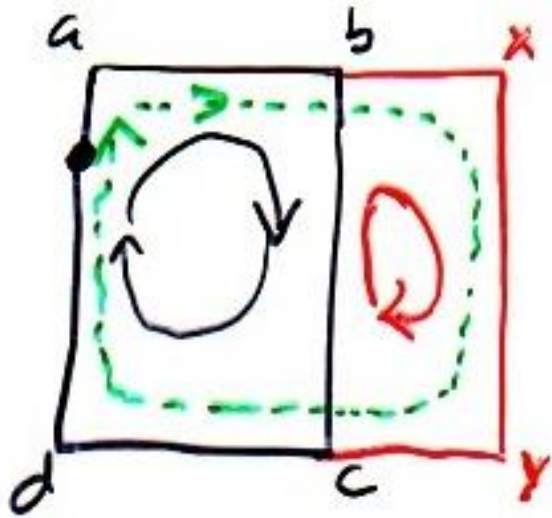- The sum of the potential difference around any closed loop is zero!



$$V_{ab} + V_{bc} + V_{cd} + V_{da} = 0$$

$$V_{bx} + V_{xy} + V_{yc} + V_{cb} = 0$$


$$V_{ax} + V_{xy} + V_{yd} + V_{da} = 0$$

$$V_{cb} + V_{bx}$$


Equivalently

$$V_{cdab} = V_{cyxb} = V_{cb}$$

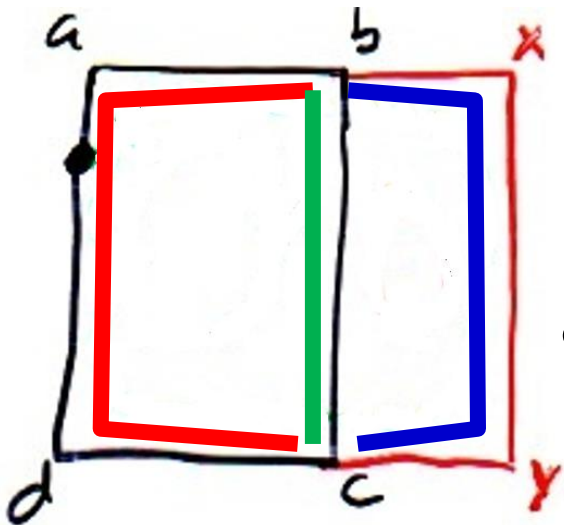- Potential difference between 2 points same for all possible paths !



Resistors in Series

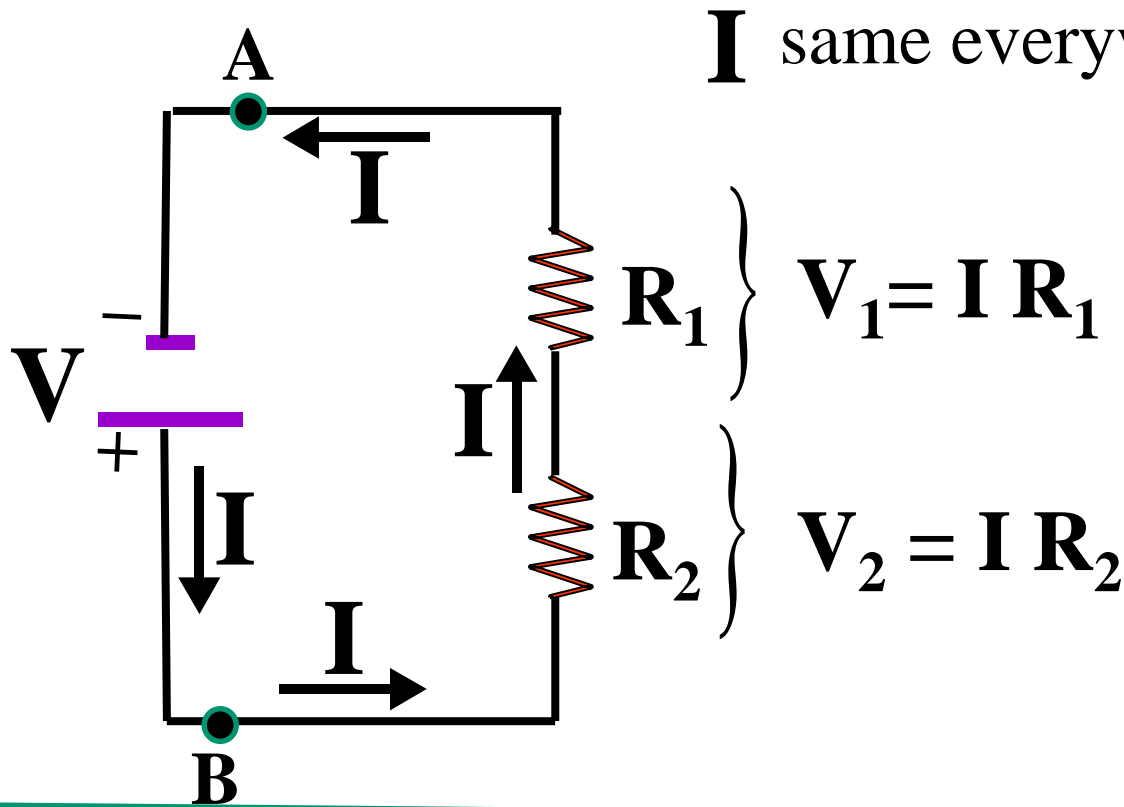

I same everywhere

$$V = V_1 + V_2$$

$$V = I R_1 + I R_2$$

$$V = I [R_1 + R_2]$$

$$V = I R_{\text{eff}}$$


$$R_{\text{eff}} = R_1 + R_2$$

in general

$$V = V_1 + V_2 + \dots + V_n = I R_{\text{eff}}$$

$$R_{\text{eff}} = R_1 + R_2 + \dots + R_n$$

Resistors in Parallel

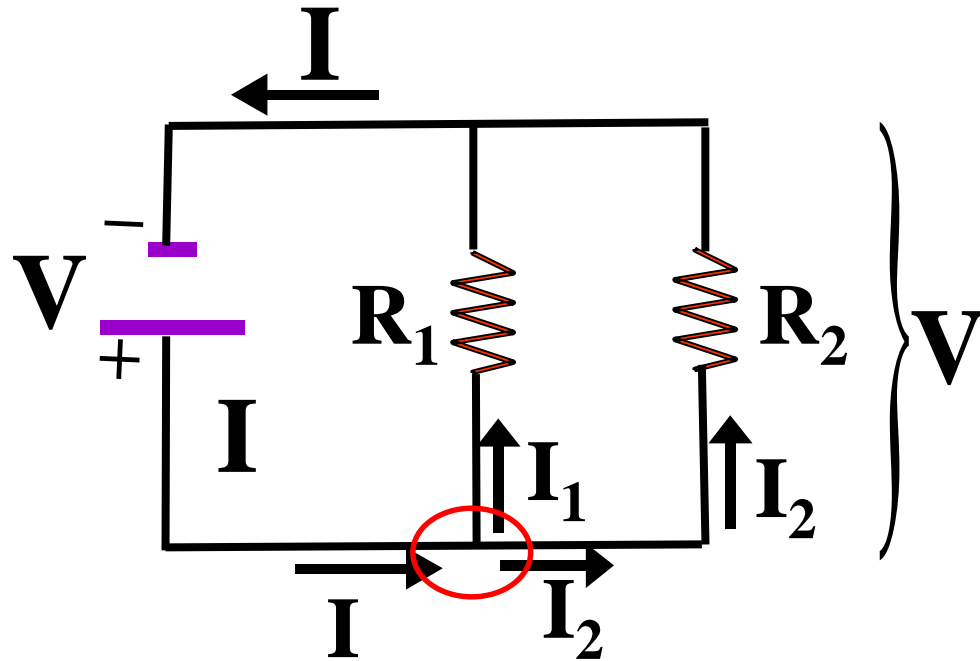

$$V = I_1 R_1 = I_2 R_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2}$$

$$I = I_1 + I_2$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} = V \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{V}{R_{eff}}$$

in general


$$V = I R_{eff}$$

$$I = \frac{V}{R_{eff}}$$

$$\frac{1}{R_{eff}} = \left[\frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$\frac{1}{R_{eff}} = \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots + \frac{1}{R_n} \right]$$

Example:

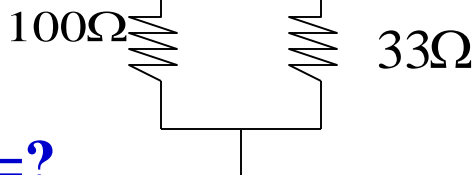

$R_{\text{reff}}=?$

$$\frac{1}{R_e} = \left[\frac{1}{100} + \frac{1}{33} \right] \left\{ \frac{1}{\Omega} \right\}$$


$$= [.01 + .03] \left\{ \frac{1}{\Omega} \right\}$$

$$\frac{1}{R_e} = .04 \frac{1}{\Omega}$$

$$R_e = \frac{1}{.04} = \frac{1}{4} (10)^2 = .25 (10)^2$$

$$R_e = 25\Omega$$

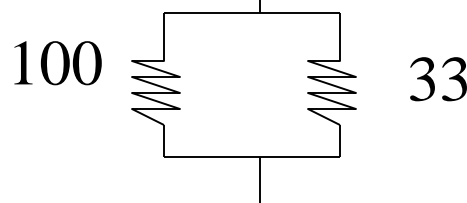Example: If $2A=I$, what is I_{33} & I_{100} ?



What is I in each leg?

$$V = I_{100}(100) = I_{33}(33) \Rightarrow I_{100} = I_{33} \frac{33}{100} = .33 I_{33}$$

$$I = I_{100} + I_{33}$$

$$I = I_{33}(.33) + I_{33}$$

$$I = I_{33}(1.33)$$

$$\frac{2}{1.33} = I_{33} \quad I_{33} = \frac{2}{4} = \frac{3}{2} = 1.5A$$

$$I_{100} = 2A - 1.5A = 0.5A$$

Symmetry approach for = parallel R's

n resistors of R in //

$R_{eff} = ?$


I sees n paths all the same

so $\frac{I}{n}$ in each path


$$V = \frac{I}{n} R$$

$$\text{or } V = I \left(\frac{R}{n} \right)$$

$$\boxed{R_{eff} = \frac{R}{n}}$$

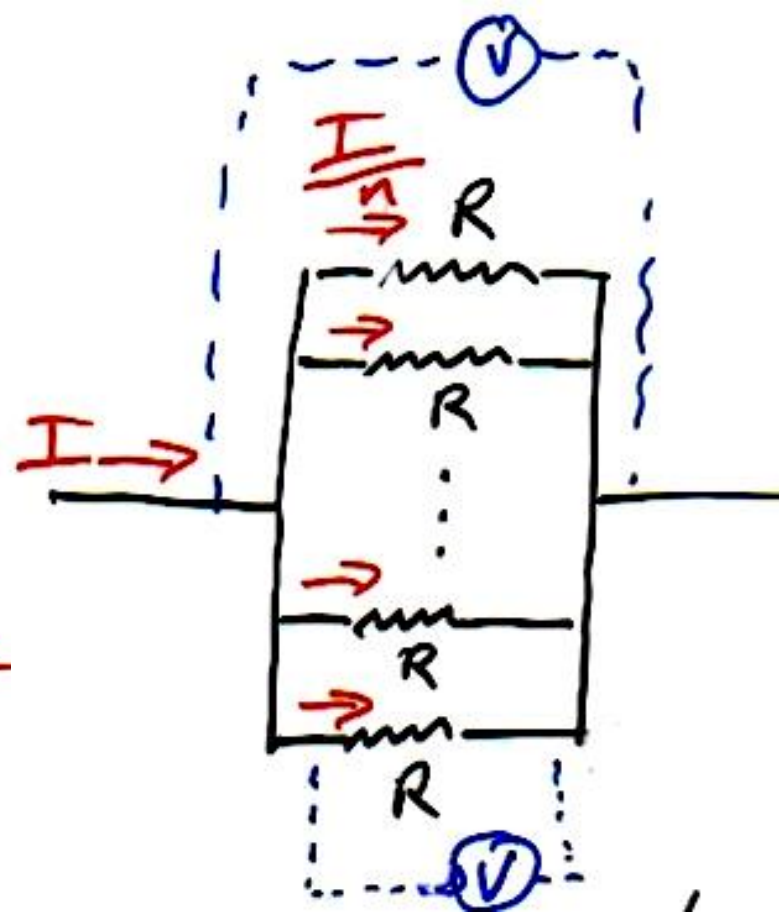

In general current ratio

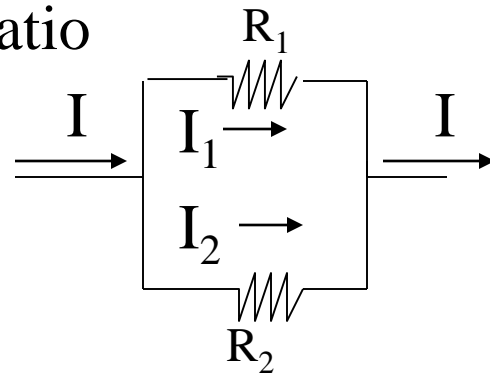

small R larger power dissipated

our example

$$I = 2A$$



$$R_1 I_1 = I_2 R_2 \Rightarrow \frac{I_2}{I_1} = \frac{R_1}{R_2} \Rightarrow I_2 = I_1 \frac{R_1}{R_2}$$

$$\frac{I_2}{I_1} = \frac{R_1}{R_2} \quad \text{Ratio of current}$$

$$\frac{I_2}{I_1} = \frac{R_1}{R_2} \quad \text{inverse ratio of R.}$$

$$I_{33}^2 R_{33} = (1.5)^2 33 = 2.25 (33)$$

$$= 74.25 \text{ Watts}$$


$$I_{100}^2 R_{100} = (0.5A)^2 100 = 0.25 100 = 25 \text{ watts}$$

$$\frac{P_2}{P_1} = \frac{I_2^2 R_2}{I_1^2 R_1} \quad \frac{P_2}{P_1} = \frac{R_2}{R_1} \left(\frac{R_1}{R_2} \right)^2$$

$$\frac{P_2}{P_1} = \frac{R_1}{R_2} \quad \text{Ratio of power}$$

$$\frac{P_2}{P_1} = \frac{R_1}{R_2} \quad \text{inverse ratio of R.}$$

R_{eff} in parallel-general observation

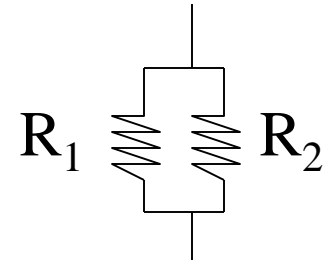

$$R_1 = 1000\Omega \quad R_2 = 100\Omega$$

$$\frac{1}{R_{\text{eff.}}} = \frac{1}{1000} + \frac{1}{100} = \frac{11}{1000}$$

$$R_{\text{eff.}} = \frac{1000}{11} = 91\Omega$$


$$\frac{1}{R_{\text{eff.}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

R_1 big \longrightarrow $R_{\text{eff.}}$ A little less
 R_2 small than R_2 (small).

Capacitors Series

$$V_1 = \frac{Q_1}{C_1}$$

$$V_2 = \frac{Q_2}{C_2}$$

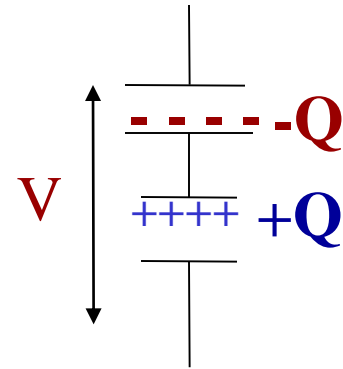

equal charge Q !!

$$V = V_1 + V_2 \rightarrow V = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$


$$\therefore V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = Q \frac{1}{C_{\text{eff}}}$$

$$\boxed{\frac{1}{C_{\text{eff}}} = \frac{1}{C_1} + \frac{1}{C_2}}$$

In general:

$$\frac{1}{C_{\text{eff}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

Capacitors Parallel

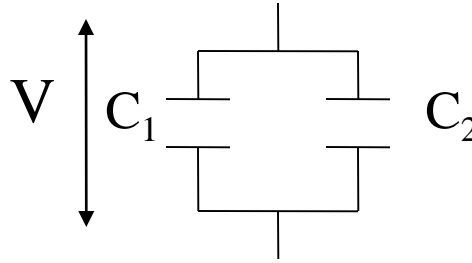

equal voltages V_s !!!

$$V C_{\text{eff.}} = Q_{\text{tot.}} = Q_1 + Q_2$$

$$V C_{\text{eff.}} = V C_1 + V C_2$$


$$C_{\text{eff}} = C_1 + C_2$$

Parallel capacitors add in general

$$C_{\text{eff}} = C_1 + C_2 + C_3 \dots\dots$$

(opposite from resistors)

like just increasing area of C

 

1.0 μf

1.5 μf


5.0 μf

Example:

$$\begin{aligned}\frac{1}{C_{\text{eff}}} &= \left(\frac{1}{1.0} + \frac{1}{1.5} + \frac{1}{5.0} \right) \left(\frac{1}{\mu f} \right) \\ &= \left(1 + \frac{1}{\frac{3}{2}} + .2 \right) \frac{1}{\mu f} = \left(1 + \frac{2}{3} + .2 \right) \frac{1}{\mu f} \\ &= (1 + .66 + .2) \frac{1}{\mu f}\end{aligned}$$

$$\frac{1}{C_{\text{eff}}} = 1.86 \frac{1}{\mu f}$$

$$C_{\text{eff}} = 0.54 \mu f$$

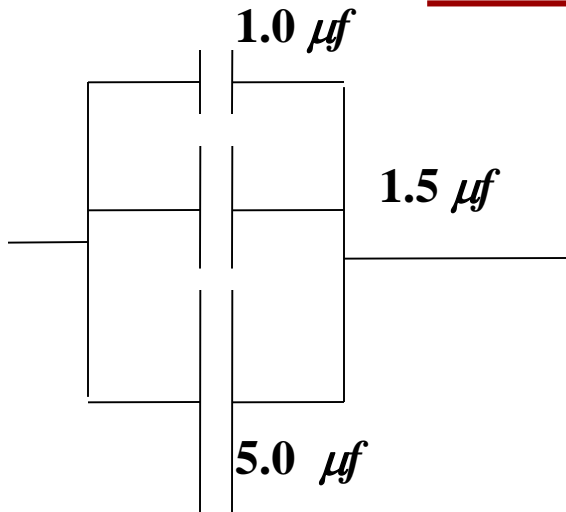

1.0 μf

1.5 μf

5.0 μf

Example:

$$C_{\text{eff}} = (1.0 + 1.5 + 5.0)(\mu f) = 7.5 \mu f$$

Exponential Function

$$f(t) = e^{-\frac{t}{\tau}}$$

τ
= time constant

$$f(t=\tau) = e^{-1} = 1/e = 1/2.718$$

$$\frac{df}{dt} = -\frac{1}{\tau} f$$

$$\frac{df}{dt} + \frac{1}{\tau} f = 0$$


$$\text{or } \frac{\Delta f}{\Delta t} = -\frac{1}{\tau} f$$

$$\frac{df}{f} = -\frac{1}{\tau} dt$$

$$\ln(f) = -\frac{t}{\tau}$$

$$\int \frac{df}{f} = -\frac{1}{\tau} \int dt$$

$$f(t) = e^{-\frac{t}{\tau}}$$

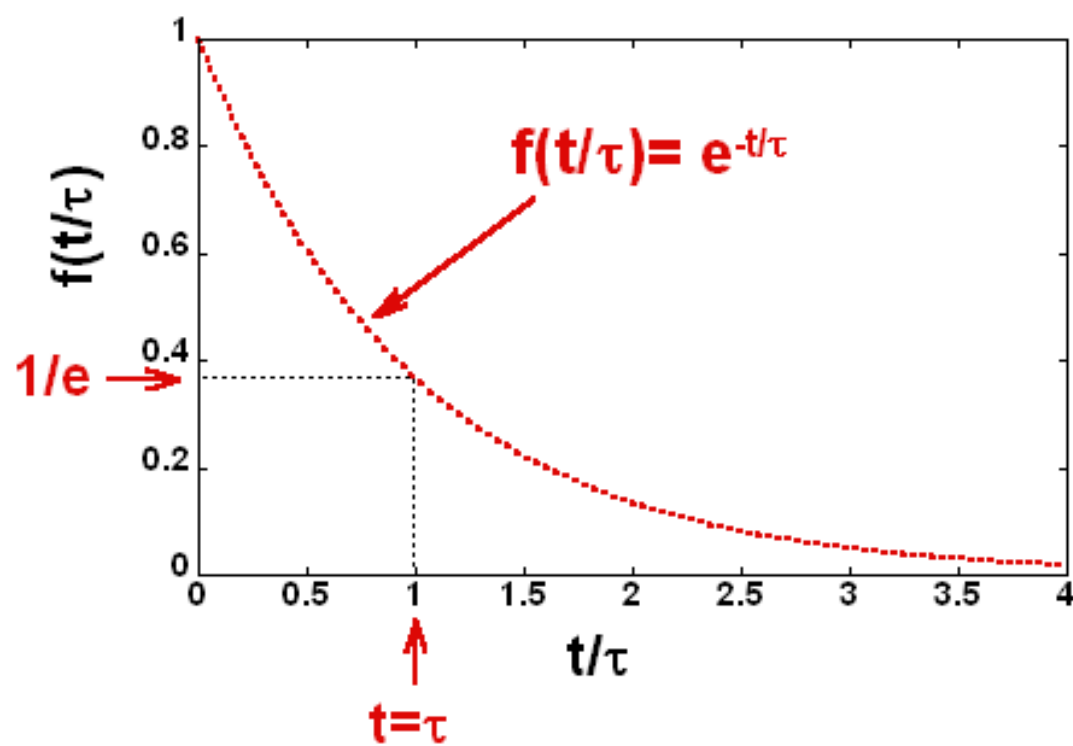


3-17

Note: gen. soln. $f(t) = f_0 e^{-\frac{t}{\tau}}$ (f_0 = constant)

Time varying electrical current

Example: Capacitor discharge

t=0 close switch

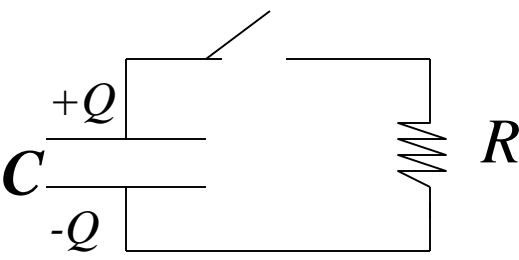

$0 = V_c + V_R$

$t=0 \quad Q=Q_0$

$0 = \frac{Q}{C} + IR$

$Q \rightarrow 0$
 $t = \infty$

$I = \frac{dQ}{dt}$

$$\frac{dQ}{dt} + \frac{Q}{[RC]} = 0$$



$\tau = RC = \text{time constant}$

$Q = [?] e^{-\frac{t}{RC}}$

$t=0 \quad Q=Q_0 \Rightarrow [?] = Q_0$


$\therefore Q = Q_0 e^{-\frac{t}{RC}}$

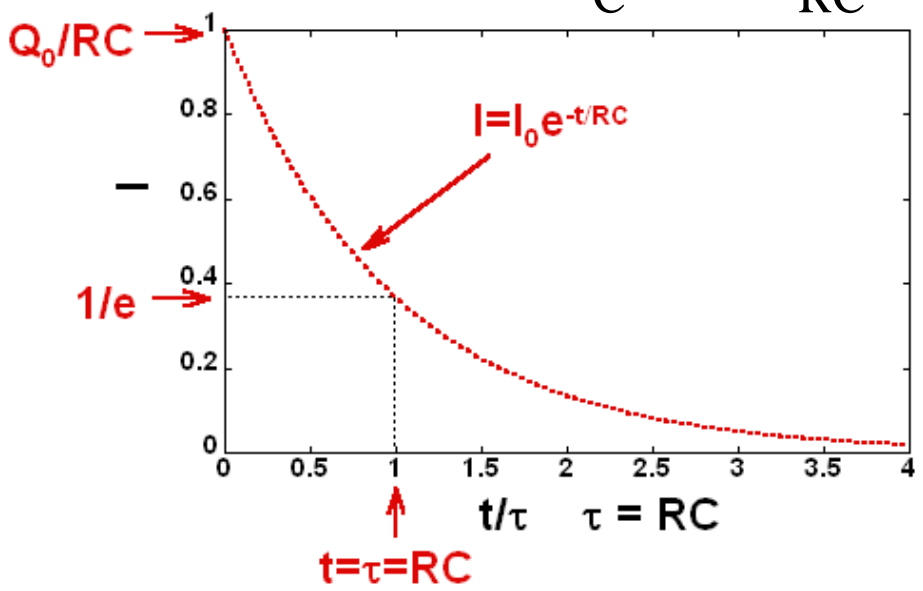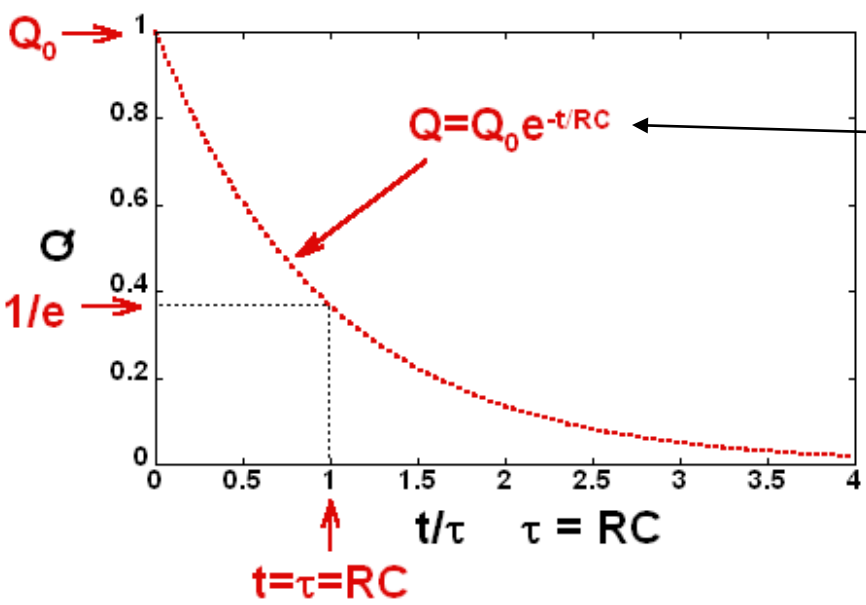Recall $IR = \frac{Q}{C} \rightarrow I = -\frac{Q}{RC}$



$$Q = Q_0 e^{-\frac{t}{RC}}$$

t=0 close switch.

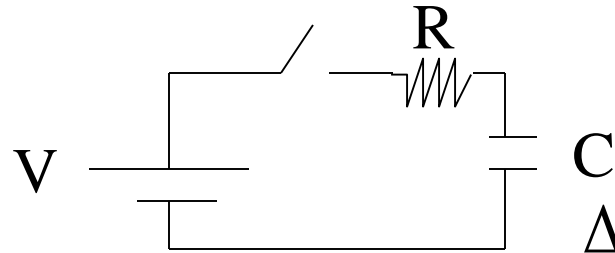

Capacitor Charging

$$-V + IR + \frac{Q}{C} = 0$$

Again: $I = \frac{\Delta Q}{\Delta t}$

$$\frac{\Delta Q}{\Delta t} R + \frac{Q}{C} = V \Rightarrow \frac{\Delta Q}{\Delta t} + \frac{Q}{RC} = \frac{V}{R} \Rightarrow \frac{dQ}{dt} + \frac{Q}{RC} = \frac{V}{R}$$

Very similar to before but not identical


t=0 Q=0: t=∞ I=0

ie. $Q_0 = VC$


$$Q = VC (1 - e^{-\frac{t}{RC}})$$

$$I = -\frac{Q}{RC} + \frac{V}{R} = -\frac{V}{R} (1 - e^{-\frac{t}{RC}}) + \frac{V}{R}$$

$$I = \frac{V}{R} e^{-\frac{t}{RC}}$$

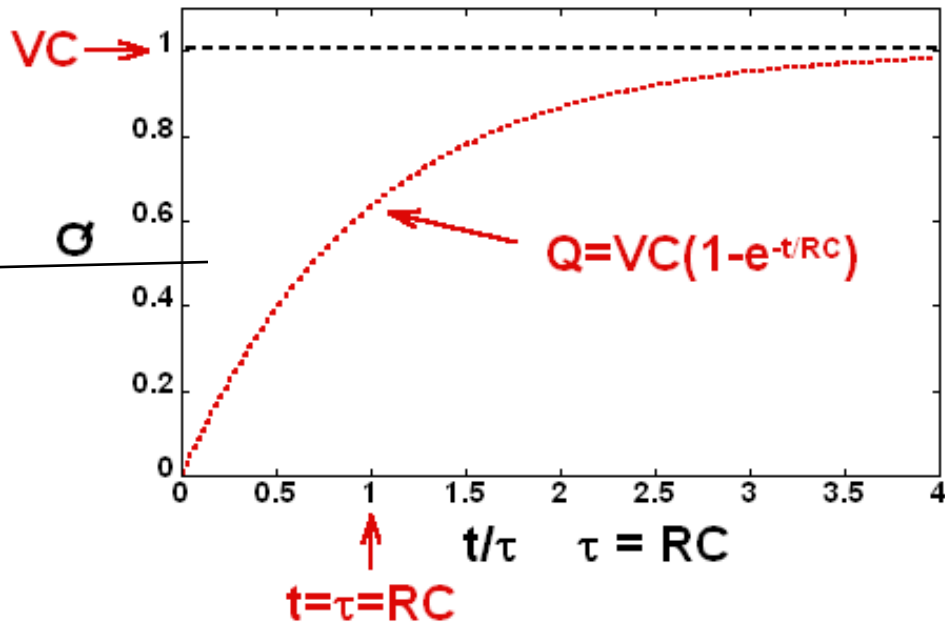

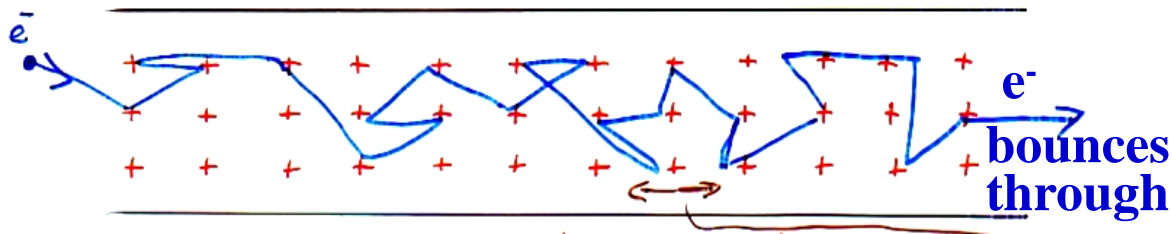
Appendix I: Temperature dependence of resistivity & superconductivity



+ atomic position (+ ions) vibrate)

- Scattering of e^- creates resistance to forward motion.

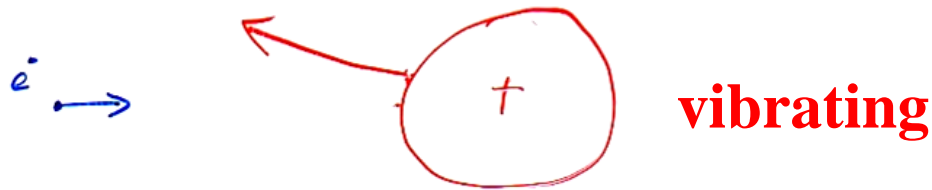- Resistance is energy loss mechanism
- ↘ motion → heat




Heavy atoms scatter **little e^-** strongly
when atoms are vibrating (at finite T).

- **Atoms vibrate less at low T**

→ Less electron scattering

→ Lower resistivity

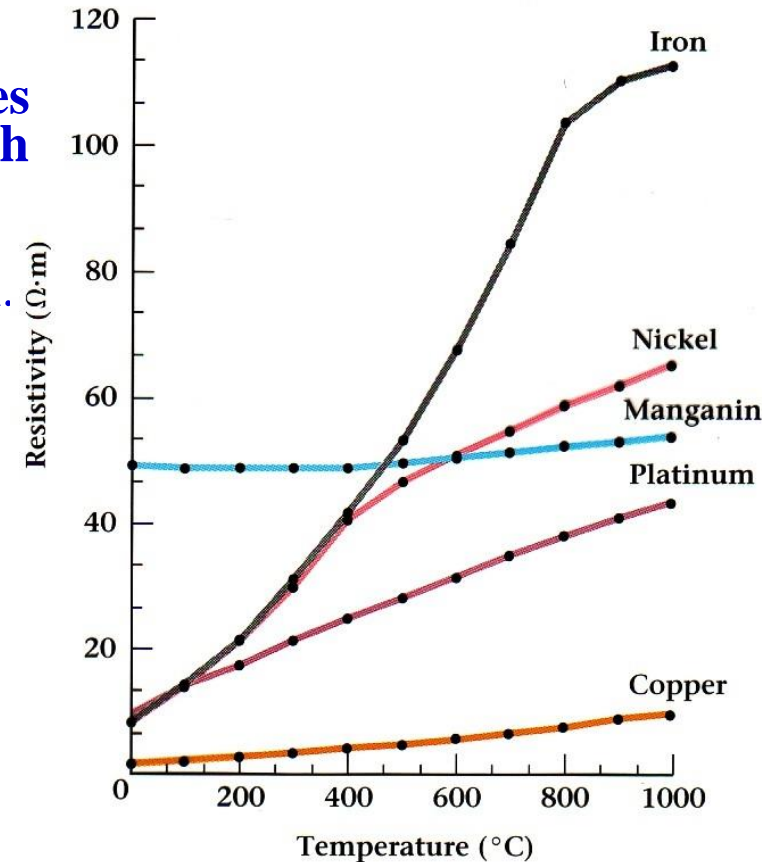

Super conductivity $R \Rightarrow 0$ at critical temp. T_c in some materials

1911-Hg $T_c=4.2\text{K}$

1950-1970 Nb_3Sn $T_c=23\text{K}$

1989 $\text{Y}_1\text{Ba}_2\text{Cu}_3\text{O}_7$ $T_c=95\text{K}$


$T_c=121\text{ K}$ highest yet!!!!

1) 2 e^- attracted to + ion

2) effective attraction between e^-

3) e^- - e^- pairs form

4) pairs don't scatter so no resistance

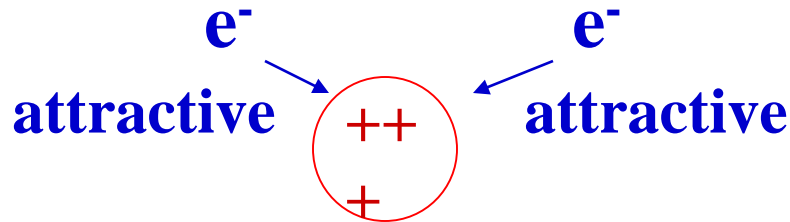

3-I-2

An infinite number of mathematicians walk into a bar.

The first one tells the bartender he wants a beer.

The second one says he wants half a beer.


The third one says he wants a fourth of a beer.

The bartender puts two beers on the bar and says “You guys need to learn your limits.”

Appendix II: Formal Kirchhoff's Laws approach/concepts

Rules

junctions

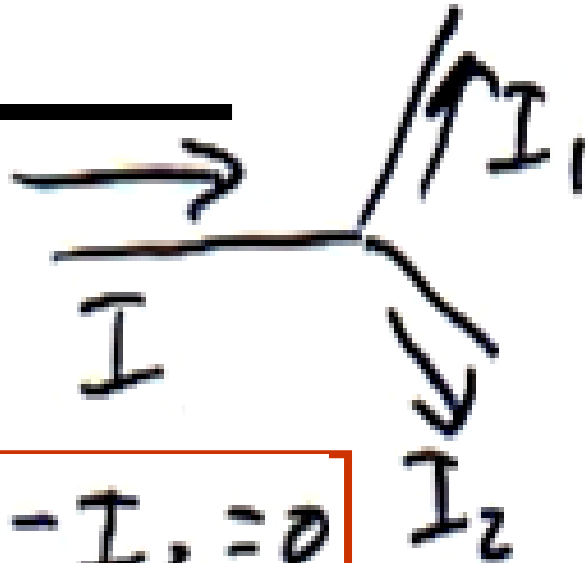

junction sign convention

+ in :: - out

(or opposite
your choice but stick to it)

$$I - I_1 - I_2 = 0$$


OR

$$I = I_1 + I_2$$

current conservation !!

= no charge build-up

Resistors: magnitude and sign convention

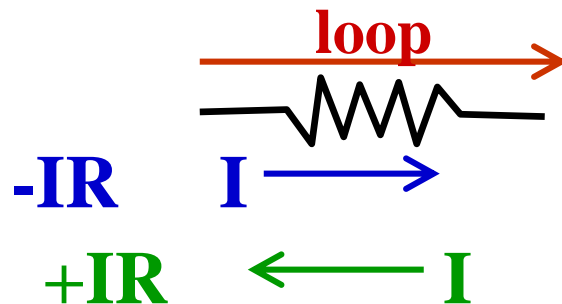


voltage drop




zero

Rules


Battery sign convention

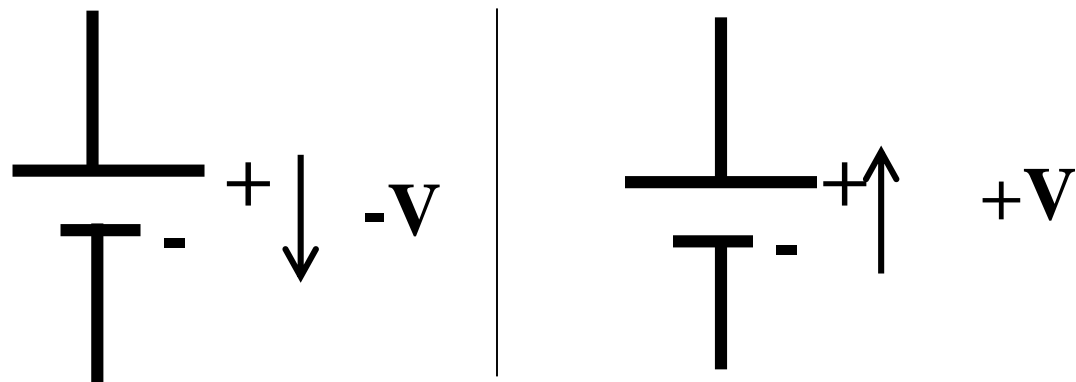

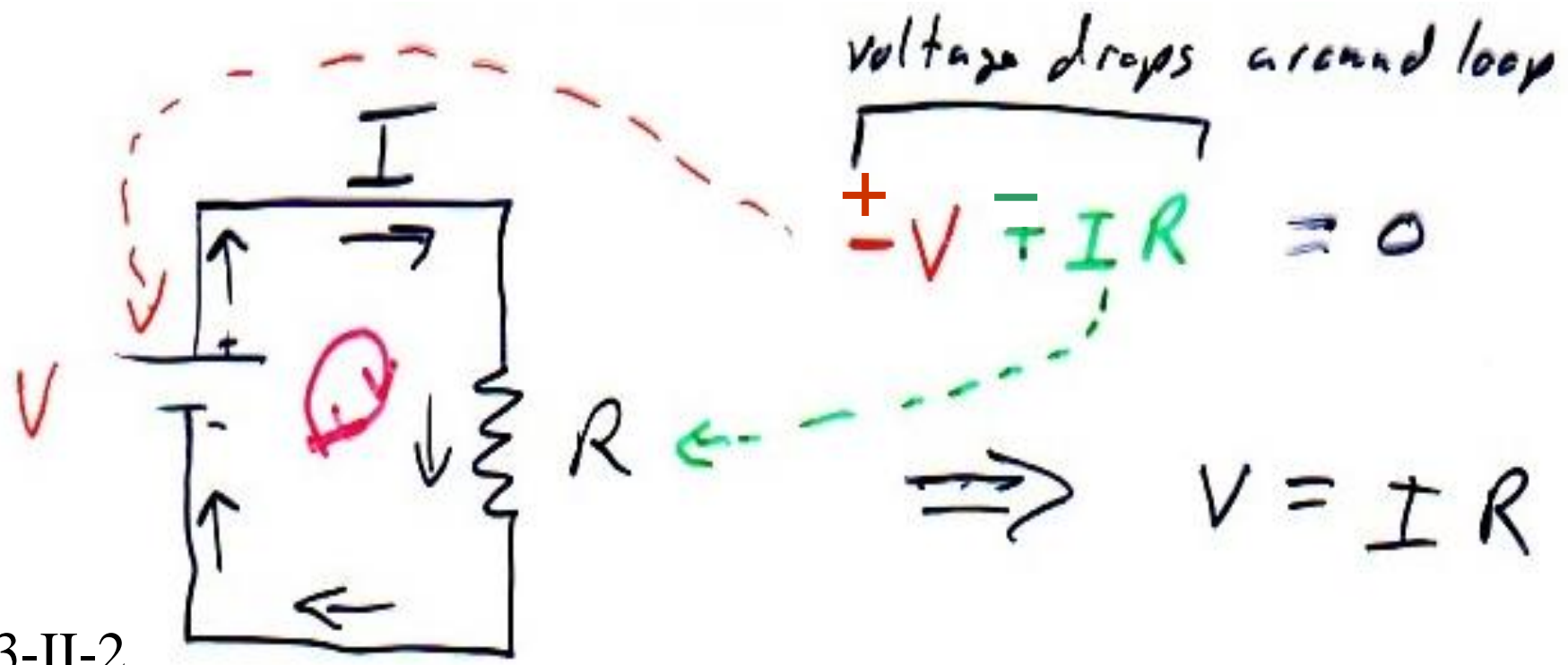Voltage drop around loop = 0 (Energy conservation !!)



Series Resistors

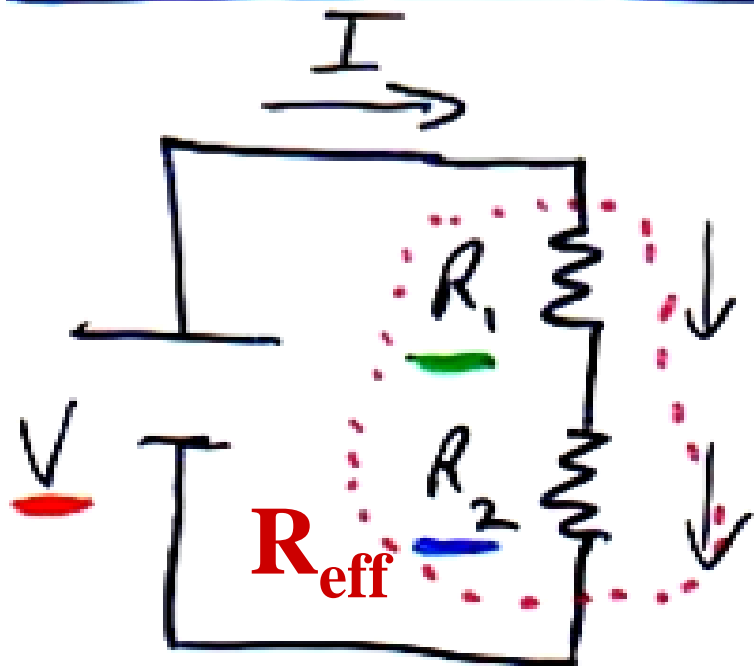

$$V - IR_1 - IR_2 = 0$$

$$V = IR_1 + R_2 I$$

$$V = I(R_1 + R_2) = I R_{eff}$$

R_{eff} - for series

In General $R_{eff} = R_1 + R_2 + R_3 + \dots$

for series resistors


Resistors in parallel

Curr. Conserv. at \oplus

$$+I - I_1 - I_2 = 0$$

in out

$$I = I_1 + I_2 \quad [1]$$

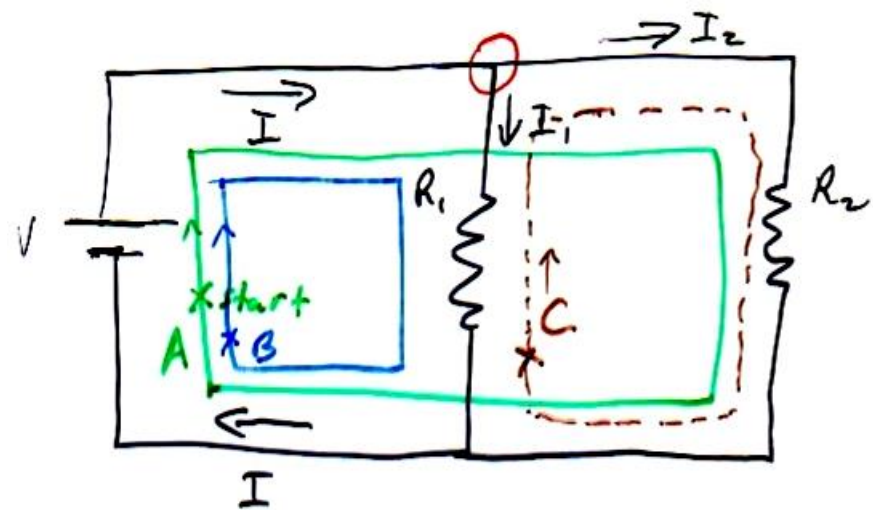

Loop A

$$+V - I_2 R_2 = 0 \rightarrow I_2 = \frac{V}{R_2} \quad [2]$$

Loop B

$$+V - I_1 R_1 = 0 \rightarrow I_1 = \frac{V}{R_1} \quad [3]$$

Loop C

$$+I_1 R_1 - I_2 R_2 = 0 \rightarrow I_1 R_1 = I_2 R_2$$

going through R_1 forwards
backwards

$$\text{or } \frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$I_2 = \frac{V}{R_2} [2]$$

[2] and [3] in [1]

$$[1] \quad I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2}$$

$$I_1 = \frac{V}{R_1} [3]$$

$$\Rightarrow I = V \left[\underbrace{\frac{1}{R_1} + \frac{1}{R_2}}_{1/R_{\text{eff}} \text{ for } //} \right] = \frac{V}{R_{\text{eff}}}$$

$$V = R_{\text{eff}} I$$

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

in general



$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \dots = \frac{1}{R_{\text{eff}}}$$